

Optimization of Robust Asynchronous Circuits by Local Input Completeness Relaxation

Cheoljoo Jeong Steven M. Nowick

Computer Science Department
Columbia University


Outline

1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks


Asynchronous Circuits

- Synchronous vs. Asynchronous Systems

Synchronous System	Asynchronous System
<i>global clock</i>	<i>no global clock</i>
entire system operates <i>at fixed rate</i>	components operate at <i>varying rates</i>
<i>centralized control</i>	<i>distributed control</i> <i>(communicate locally via handshaking)</i>

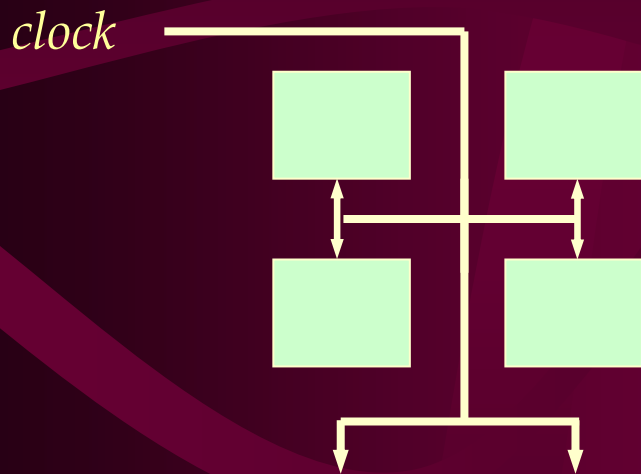

Synchronous System

 

Asynchronous System

Asynchronous Circuits (cont.)

- **Benefits of Asynchronous Circuits**

- Robustness to process variation
- Mitigates: timing closure problem
- Low power consumption, low EMI
- Modularity

- **Challenges in Asynchronous Circuit Design**

- Lack of CAD tools
- Robust design is required: hazard-freedom
- Area overhead
- Lack of systematic optimization techniques

Unoptimized Asynchronous Synthesis Flow

- Existing Synthesis Flow:

Single-rail Boolean network

*Considered as
abstract multi-valued circuit*




dual-rail expansion (delay-insensitive encoding)

Dual-rail asynchronous circuit

*Instantiated Boolean circuit
(robust, **unoptimized**)*

Single-Rail Boolean Networks

 - Boolean Logic Network: *Starting point for dual-rail circuit synthesis*
 - Uses three-valued logic with {0, 1, NULL}
 - 0/1 = data values
 - NULL = no data (invalid data)
 - Computation alternates between *DATA and NULL phases*




- DATA (Evaluate) phase:
 - outputs have DATA values only after all inputs have DATA values
- NULL (Reset) phase:
 - outputs have NULL values only after all inputs have NULL values.

Delay-Insensitive Encoding

- Approach:

 - Single Boolean signal is represented by two wires (0-rail and 1-rail)
- Goal: map abstract Boolean netlist to robust dual-rail asynchronous circuit



a_1	a_0	a
0	0	NULL
0	1	0
1	0	1
1	1	<i>Not allowed</i>

spacer

valid data

invalid

Encoding table


- Motivation: robust data communication

Dual-Rail Expansion

- Approach:
 - Goal: To obtain dual-rail circuit
 - dual-rail implementation of Boolean network
 - Single Boolean signal: is represented by two wires (0-rail / 1-rail)
 - Single Boolean gate: expanded into small dual-rail network
- Two common dual-rail circuit styles
 - DIMS (Delay-Insensitive Minterm Synthesis)
 - NCL (Null Convention Logic)


Dual-Rail Asynchronous Circuits

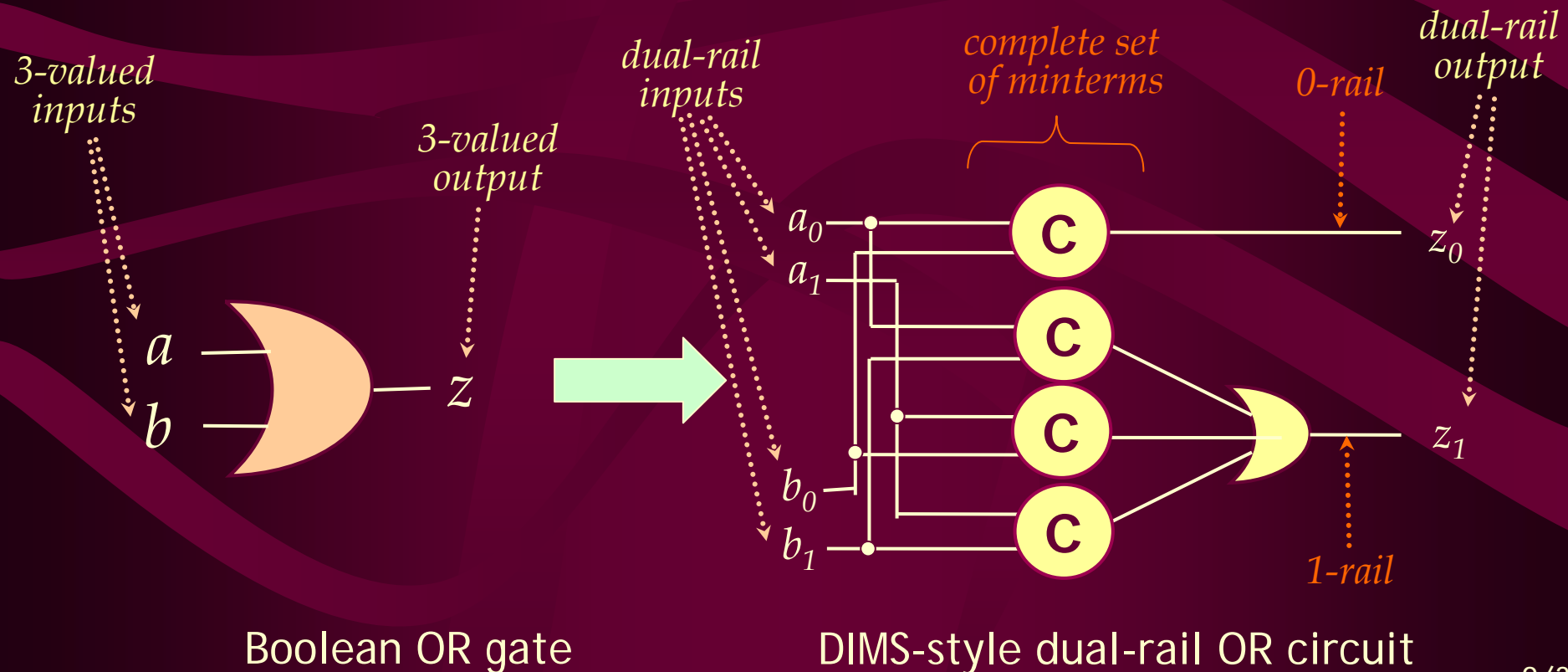- DIMS-Style Dual-Rail Expansion:
 - Single Boolean gate: expanded into 2-level network




Dual-Rail Asynchronous Circuits (cont.)

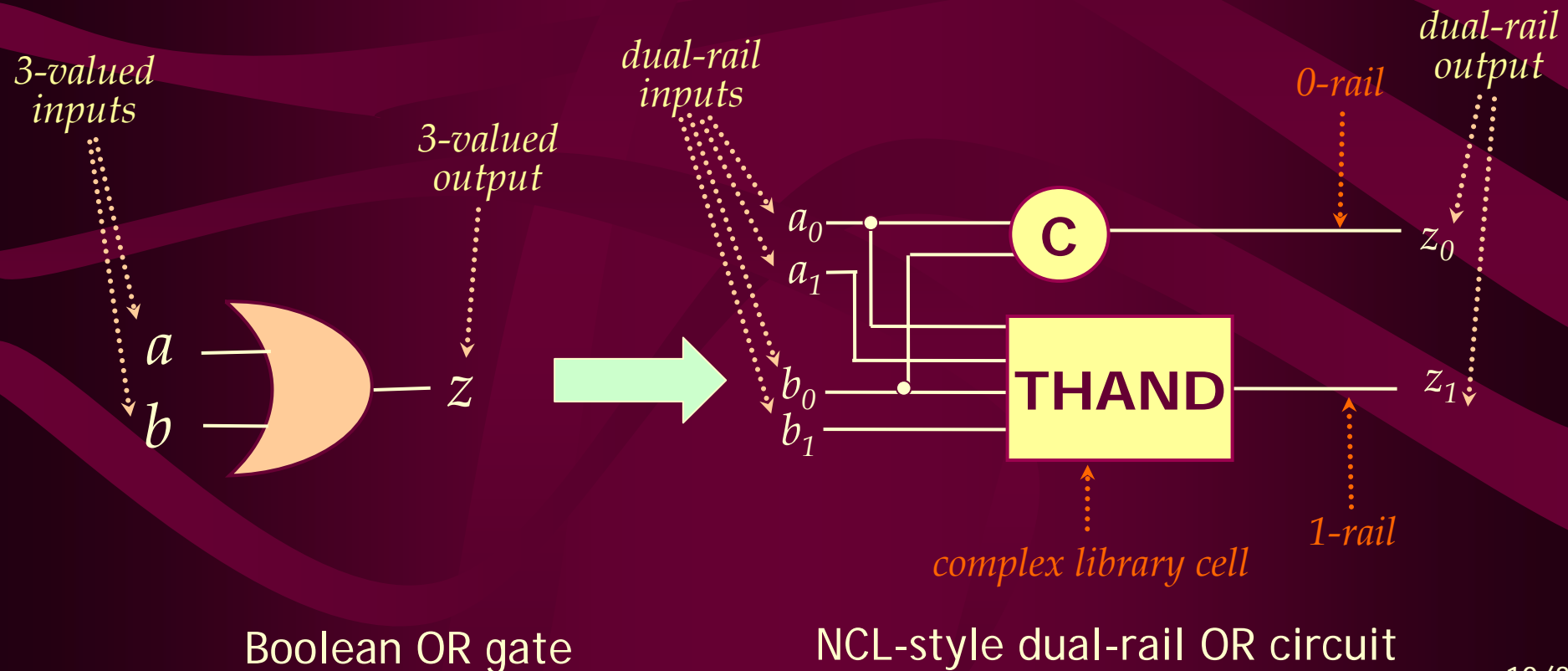- NCL-Style Dual-Rail Expansion (*Theseus Logic*):
 - Single Boolean gate: expanded into two NCL gates
 - Allows more optimized mapping (to custom library)




Summary: Existing Synthesis Approach

 - Starting Point: single-rail abstract Boolean network (3-valued)
- Approach: performs dual-rail expansion of each gate
 - Use 'template-based' mapping (DIMS-style, NCL-style)
- End Point: (unoptimized) dual-rail asynchronous circuit
- Result: timing-robust asynchronous netlist



Boolean logic network

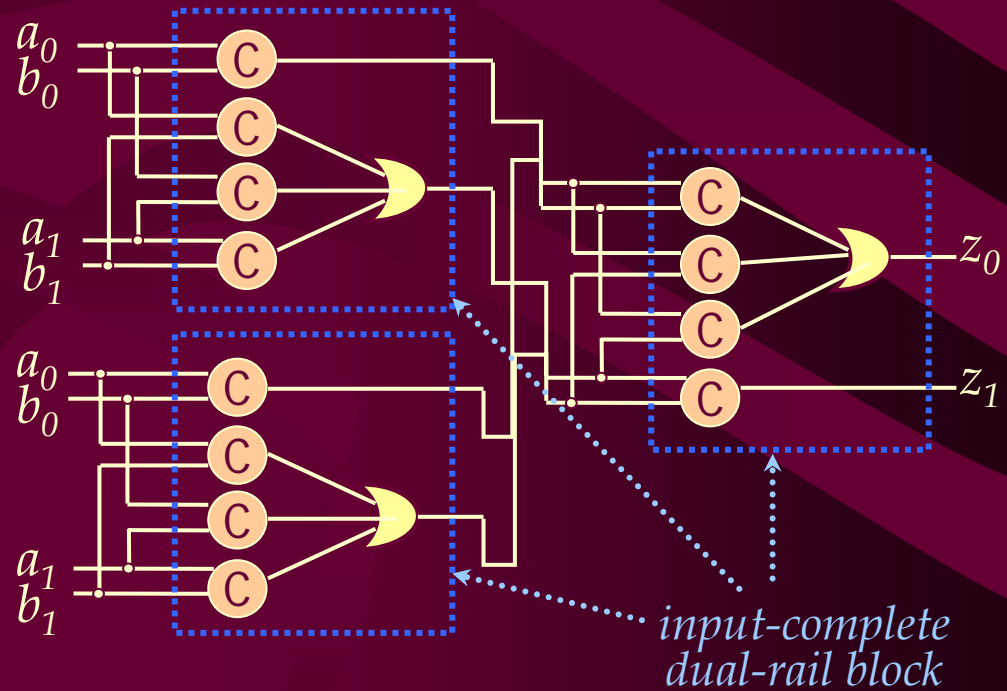


Dual-rail asynchronous circuit

*input-complete
dual-rail block*

Summary: Proposed Optimized Approach

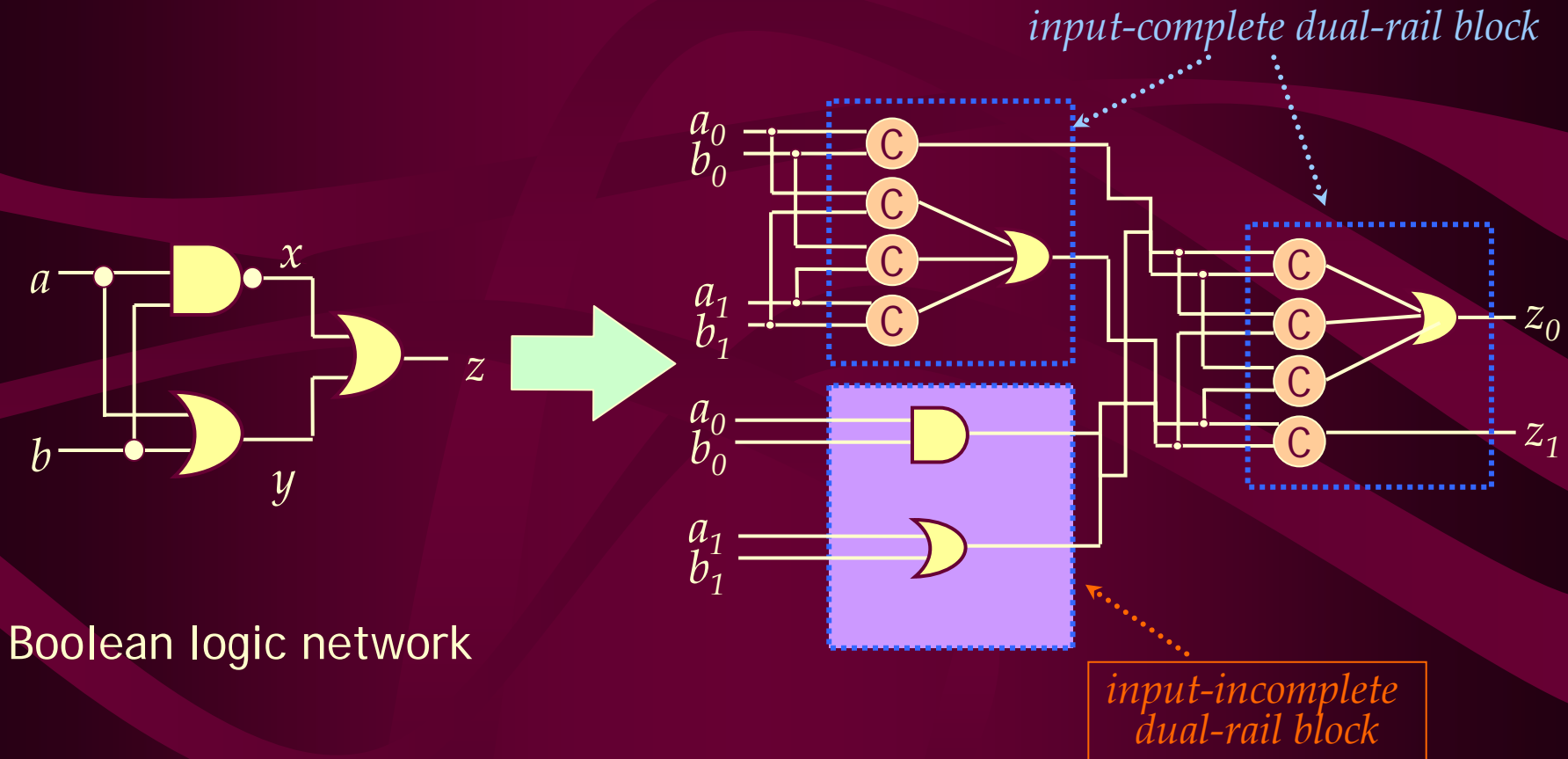- Dual-rail circuit example (with *gate relaxation*) :



Boolean logic network

Relaxed (= "eager") dual-rail asynchronous circuit

Outline


1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks

Hazard Issues

- Delay-Insensitivity (= Delay Model)
 - Assumes arbitrary gate and wire delay
 - circuit operates correctly under all conditions
 - Most robust design style
- "Orphans": Hazards to Delay-Insensitivity
 - "*Ineffective*" signal transition sequences
(= *unobservable paths*)
 - *Wire orphans*: timing requirements on wires at fanout
 - *Gate orphans*: timing requirements on paths at fanout

Hazard Issues (cont.)


- Wire Orphan Example:

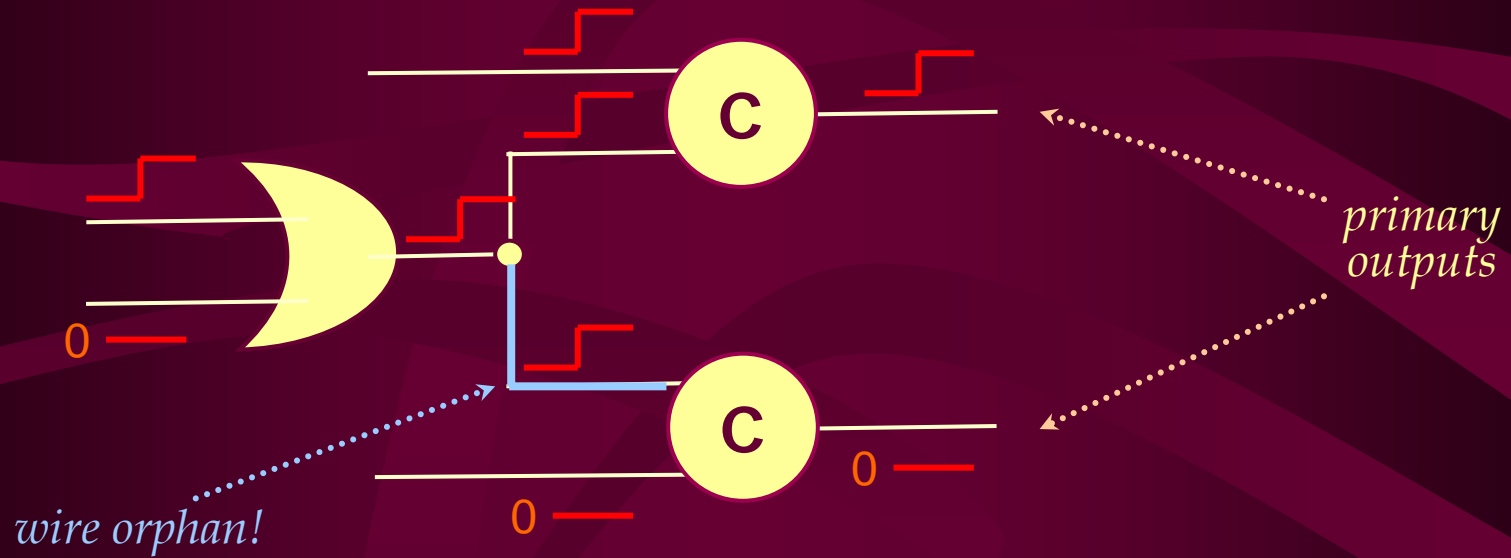

Wire orphan example

Hazard Issues (cont.)

- Gate Orphan Example:

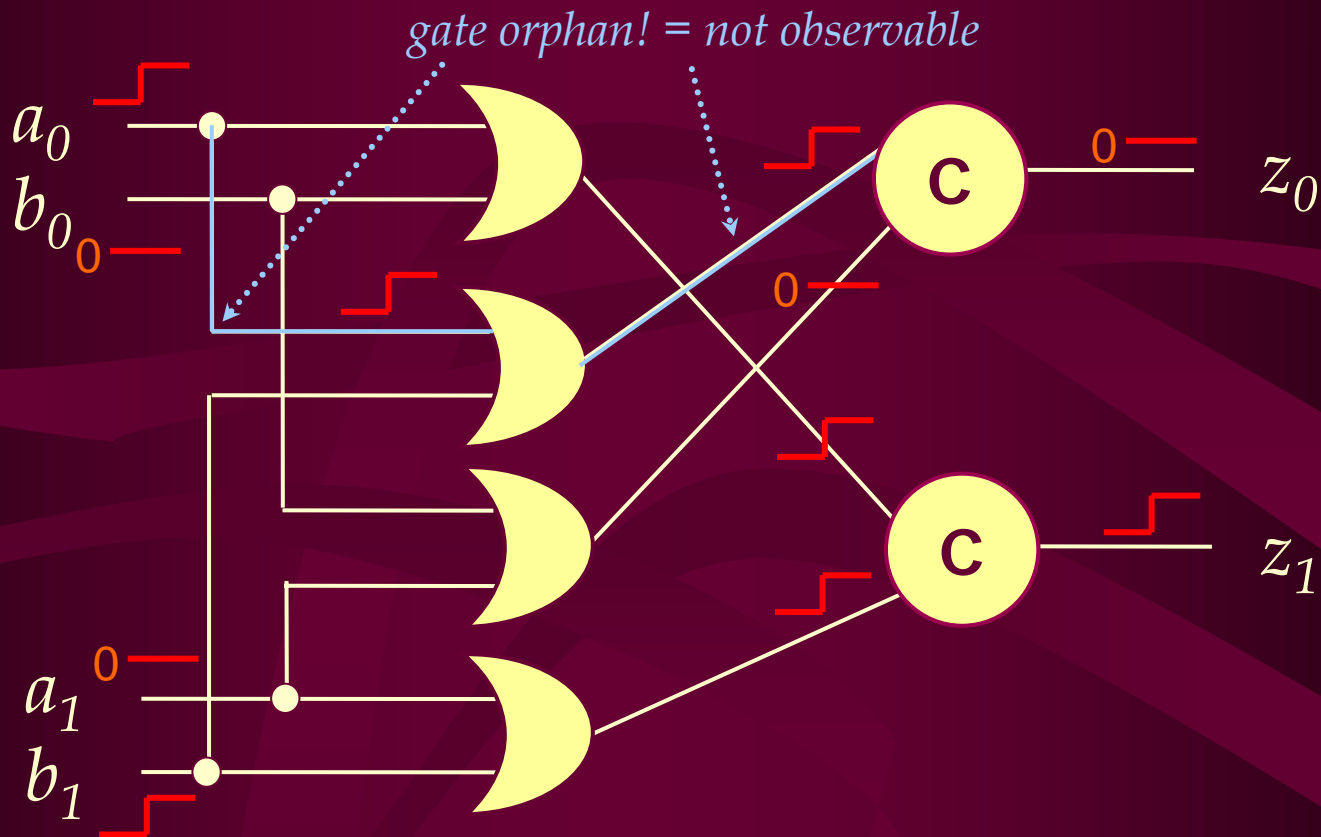


Gate orphan example

Timing-Robustness of Dual-Rail Circuits


- Wire Orphans: not a problem in practice
 - ⇒ Eliminated by enforcing physical timing constraints
 - **Option #1:** Isochronic fork timing requirement
 - At each fanout point: make every fanout delay nearly identical
 - **Option #2:** Loop timing requirement
 - At each fanout point: make every fanout delay less than time-to-reset
- Gate Orphans: challenge to robust circuit design
 - ⇒ Must avoid introducing gate orphans during synthesis
 - our goal

Input Completeness

 - A dual-rail implementation of a Boolean gate is input-complete w.r.t. its input signals if an output changes *only after* all the inputs arrive.



Boolean OR gate

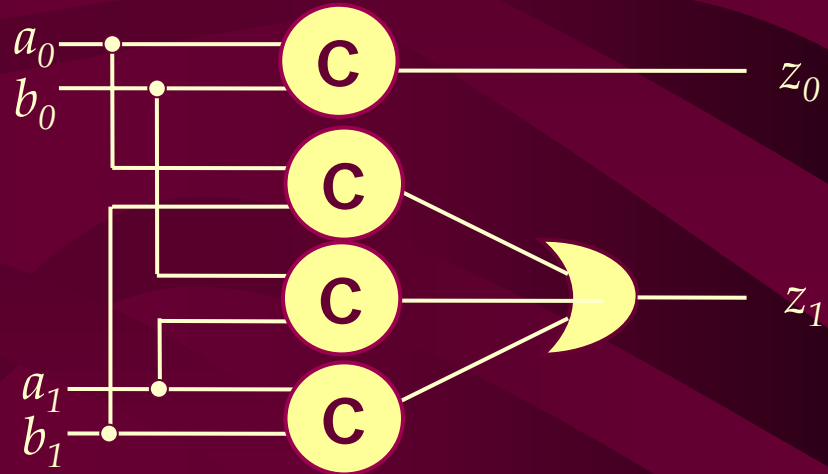


Input-complete dual-rail OR network

(input complete w.r.t. input signals a and b)



Enforcing input completeness for every gate is the traditional synthesis approach to avoid gate orphans.

Input Completeness (cont.)

 - In *input-incomplete* (i.e. "eager-evaluating") blocks, output can fire before all inputs arrive.



Boolean OR gate

  


Input-incomplete dual-rail OR network

Outline

 
1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks

Motivational Example #1

- Existing approach to dual-rail expansion is too restrictive.
 - Every Boolean gate is fully-expanded into an *input-complete* block.




Boolean network

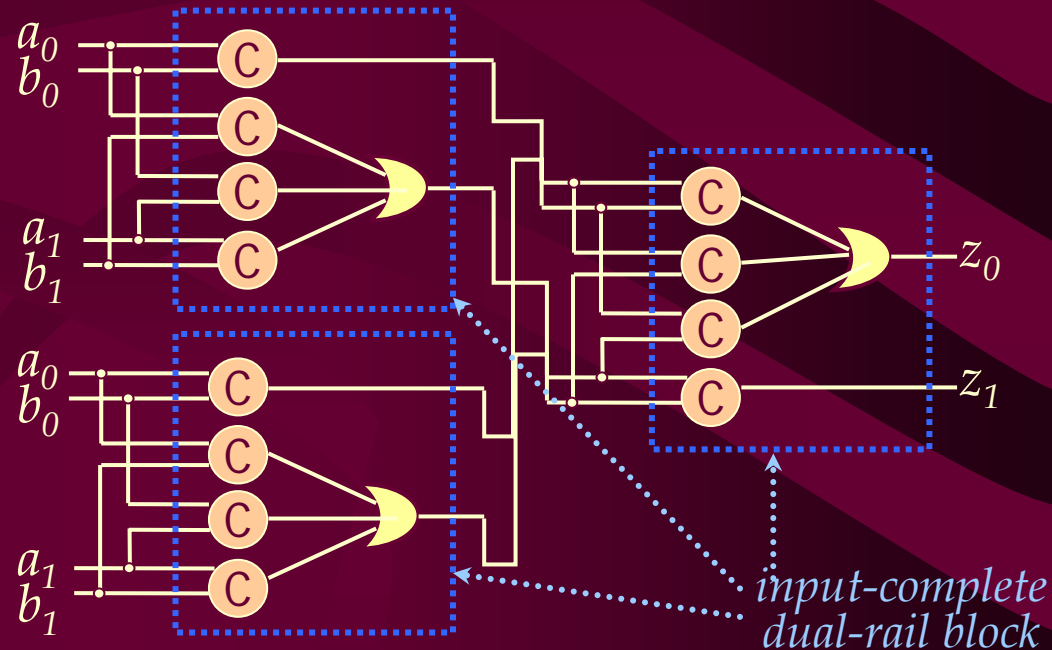

Dual-rail circuit with full expansion (no relaxation)

Motivational Example #1 (cont.)

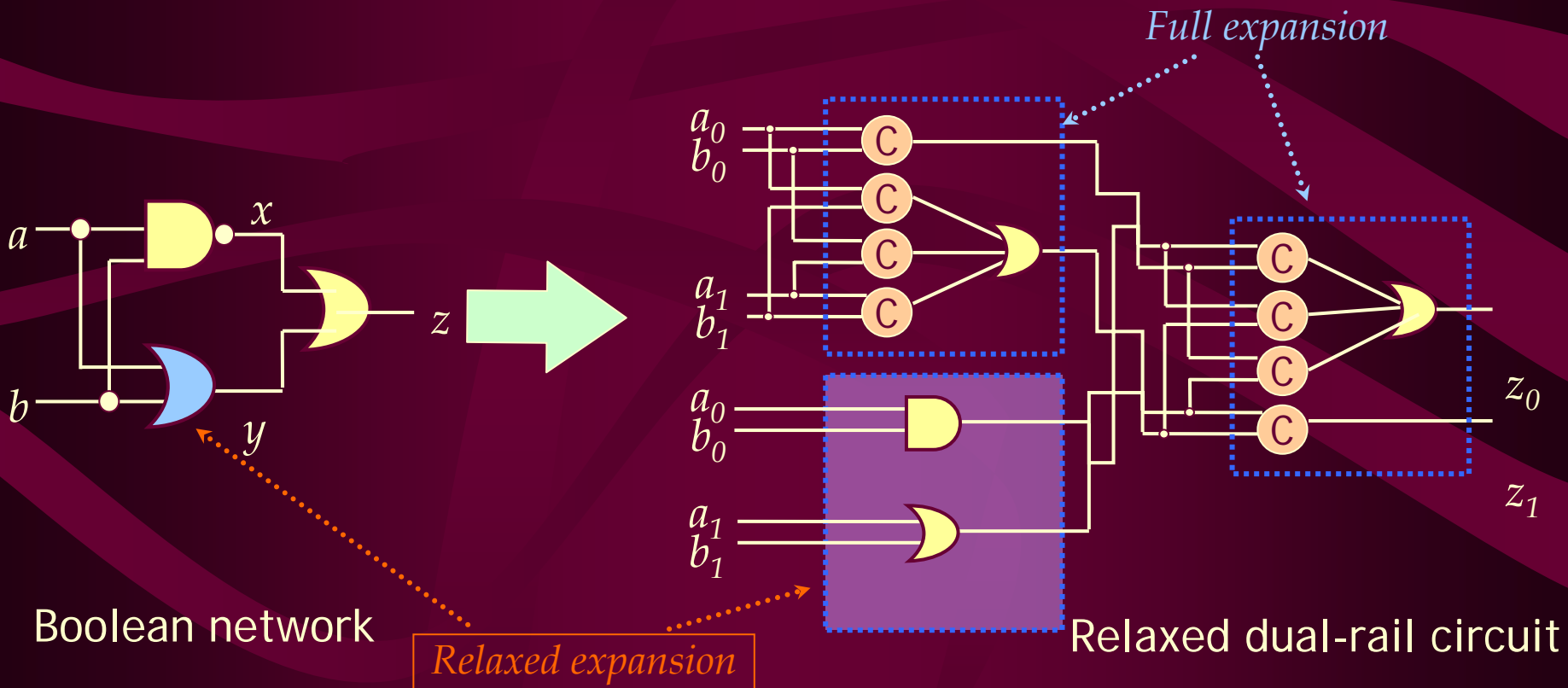
- Not every Boolean gate needs to be expanded into input-complete block.



Optimized dual-rail circuit is still robust (gate-orphan-free)

Motivational Example #2

 
- Different choices may exist in relaxation.



Relaxation of Boolean network with two relaxed gates

Motivational Example #2 (cont.)

 - Different choices may exist in relaxation.



Relaxation of Boolean network with four relaxed gates


Outline

1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks

Input Completeness Relaxation

- Theorem: *Dual-rail implementation of a Boolean network is timing-robust (i.e. gate-orphan-free) if and only if, for each signal, at least one of its fanout gates is not relaxed (i.e. ensures input completeness).*

- Example:

 


Boolean network

Input Completeness Relaxation

- Theorem: *Dual-rail implementation of a Boolean network is timing-robust (i.e. gate-orphan-free) if and only if, for each signal, at least one of its fanout gates is not relaxed (i.e. ensures input completeness).*

- Example:

 


Boolean network

Two fanout gates for signal a

Input Completeness Relaxation

- Theorem: *Dual-rail implementation of a Boolean network is timing-robust (i.e. gate-orphan-free) if and only if, for each signal, at least one of its fanout gates is not relaxed (i.e. ensures input completeness).*

- Example:

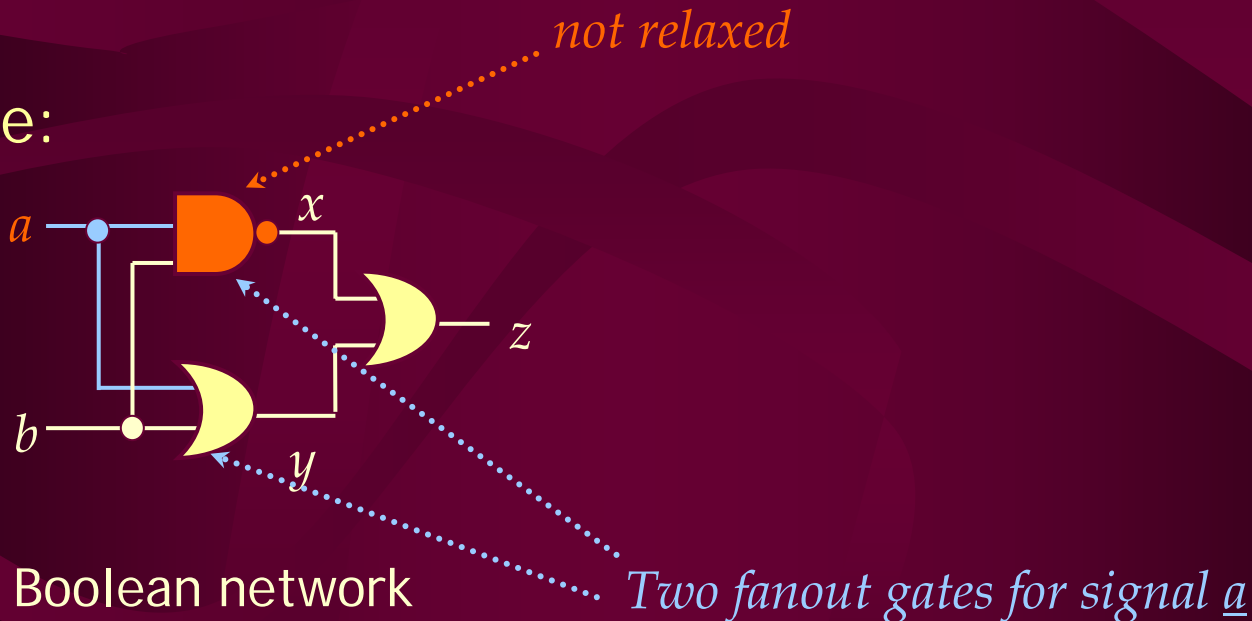

Only one of two fanout gates needs to be input-complete.

Outline

1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks


Problem Definition

- The Input Completeness Relaxation Problem
 - Input: single-rail Boolean logic network
 - Output: relaxed dual-rail asynchronous circuit, which is still timing-robust
- Overview of the Proposed Algorithm
 - Relaxes overly-restrictive style of existing approaches
 - Performs selective relaxation of individual nodes
 - Targets three cost functions:
 - Number of relaxed-gates
 - Area after dual-rail expansion
 - Critical path delay
 - Based on *unate covering framework*:
 - Each gate output must be covered by at least one fanout gate


Relaxation Algorithm

- Algorithm Sketch

 - Step 1: setup covering table
 - For each pair $\langle u, v \rangle$, signal u fed into gate v :
 - Add u as a covered element (row)
 - Add v as a covering element (column)
- Step 2: solve unate covering problem



Boolean network

 

signals

gates

	X	Y	Z
a	1	1	0
b	1	1	0
x	0	0	1
y	0	0	1

Covering table

Targeting Different Cost Functions

- Maximization of Number of Relaxed Gates
 - Weight of a gate = 1
- Minimization of Area of Dual-Rail Circuit
 - Weight of a gate = area penalty for not relaxing the gate
- Critical Path Delay Optimization in Dual-rail Circuit
 - Find a critical path in non-relaxed dual-rail circuit
 - Assign higher weights to critical gates
 - Assign lower weights to non-critical gates
 - GOAL: more relaxation of critical path gates

Outline

1. Introduction
2. Background: Hazard Issues
3. Motivational Examples
4. Theorem on Input Completeness
5. Relaxation Algorithm
6. Experimental Results
7. Concluding Remarks

Experimental Results

- Results for DIMS-style asynchronous circuits

Original Boolean network		Unoptimized DIMS circuit			Optimization Run		
					# Relaxed nodes min.	Area min.	Delay opt.
name	#i/#o/#g	# full blocks	area	delay	# full blocks	area	delay
C1908	33/25/462	343	94532	30.0	180	58618	25.9
C3540	50/22/1147	911	281918	46.0	476	189612	38.7
C5315	178/123/1659	1259	335801	32.7	727	235391	28.5
C6288	32/32/3201	2385	567010	133.6	1246	361478	106.1
C7552	207/108/2155	1677	427101	44.8	1042	305203	43.4
dalu	75/16/756	633	201912	20.0	346	144288	14.8
des	256/245/2762	2329	712145	23.2	1157	462165	19.5
K2	45/43/684	597	222326	18.9	289	131498	14.0
t481	16/1/510	476	154466	20.8	211	99514	17.5
vda	17/39/383	309	121947	17.7	137	69231	15.7
Average percentage					51.8%	65.1%	83.9%

(selected MCNC combinational benchmarks)

Experimental Results


- Results for NCL asynchronous circuits
- *(style used at Theseus Logic)*

Original Boolean network		NCL circuit			Optimization Run		
					# Relaxed nodes min.	Area min.	Delay opt.
name	#i/#o/#g	# full blocks	area	Delay	# full blocks	area	delay
C1908	33/25/462	343	55940	33.3	180	37917	28.3
C3540	50/22/1147	911	189970	51.0	476	147575	42.8
C5315	178/123/1659	1259	189370	36.4	727	154238	31.0
C6288	32/32/3201	2385	264750	151.1	1246	203490	123.0
C7552	207/108/2155	1677	224790	48.8	1042	180362	46.9
dalu	75/16/756	633	140190	21.7	346	113949	15.5
des	256/245/2762	2329	364812	24.8	1157	358692	20.9
K2	45/43/684	597	175590	20.2	289	108765	14.8
t481	16/1/510	476	109000	22.1	211	84655	17.7
vda	17/39/383	309	100230	19.0	137	60214	15.7
Average percentage					51.8%	74.1%	82.3%

(selected MCNC combinational benchmarks)

Experimental Results

 - **Minimizing Number of Relaxed Nodes:**
 - DIMS circuits: 48.2% relaxed
 - NCL circuits: 48.2% relaxed
- **Area minimization:**
 - DIMS circuits: 34.9% improvement
 - NCL circuits: 25.9% improvement
- **Critical Path Delay optimization:**
 - DIMS circuits: 16.1% improvement
 - NCL circuits: 17.7% improvement



No change to overall timing-robustness of circuits


Related Work

- Two approaches to relaxation
 - Relax every gate but add local completion detectors
 - Relax selectively with no additional circuitry
- Approach #1: Relax every gate
 - David et al. *An Efficient Implementation of Boolean Circuits as Self-Timed Circuits*, IEEE Trans. Computers 1992
 - (+) More relaxation opportunities
 - (-) Overhead of additional circuitry to ensure robustness
- Second approach: Selective relaxation
 - Smith et al. *Optimization of Null Convention Self-Timed Circuits*, Integration 2004
 - (+) No overhead of additional circuitry
 - (-) No general relaxation algorithms
 - Zhou et al. *Cost-aware Synthesis of Asynchronous Circuits Based on Partial Acknowledgement*, ICCAD 2006
 - Related approach (developed in parallel independently)

Conclusion

- **Input Completeness Relaxation Algorithm**

 - Optimization technique for robust "asynchronous" circuits
- Relaxes overly-restrictive style of existing approaches
- Can target three different cost functions:
 - # Relaxed nodes, area, critical path delay
- CAD tool developed
- Significant improvement:
 - Average relaxation of 48.2% of gates
 - Average area improvement of up to 34.9%
 - Average delay improvement of up to 17.7%



No change to overall timing-robustness of circuits

- **Future Work**

- More sophisticated delay optimization scheme
- More fine-grained relaxation schemes: e.g. independent consideration of set/reset phases