

Efficient Synthesis of Compressor Trees on FPGAs


Hadi Parandeh-Afshar^{1,2}

Philip Brisk²

Paolo Ienne²

1: University of Tehran, ECE Department

 2: EPFL, School of Computer and Communication Sciences





Outline

- State of the Art: FPGAs
- Motivation
- Generalized Parallel Counters
- Mapping Heuristic
- Experimental Results
- Conclusion



Outline

- State of the Art: FPGAs
- Motivation
- Generalized Parallel Counters
- Mapping Heuristic
- Experimental Results
- Conclusion

FPGA vs. ASIC



	ASIC	FPGA
Performance	✓	
Area Utilization	✓	
Power Consumption	✓	
Flexibility		✓
Time-to-Market		✓



FPGA Arithmetic Features

- Poor Performance for Arithmetic Operations Compared to ASIC
- IP Cores
 - High Routing Costs
 - Limited Flexibility; 18-bit Adder/Multiplier
- Full Adder Implemented in CLB Structure
 - Fast Carry-Chain (Xilinx and Altera)
 - Reduces Routing Delay
 - Cannot Use Compressor Trees to Add $k > 2$ Values
 - Wallace/Dadda/3-Greedy



Outline


- State of the Art: FPGAs
- **Motivation**
- Generalized Parallel Counters
- Mapping Heuristic
- Experimental Results
- Conclusion




Motivation

- Arithmetic dominated circuits such as multimedia and signal processing
 - Multi-input ADD is inherently a frequent operation
 - ADD and MULT are dominant operations
 - Using [Verma-lenne] transformations to integrate disperse operations
 - Accelerating multi-input additions

Verma-lenne Transformation [ICCAD '04]

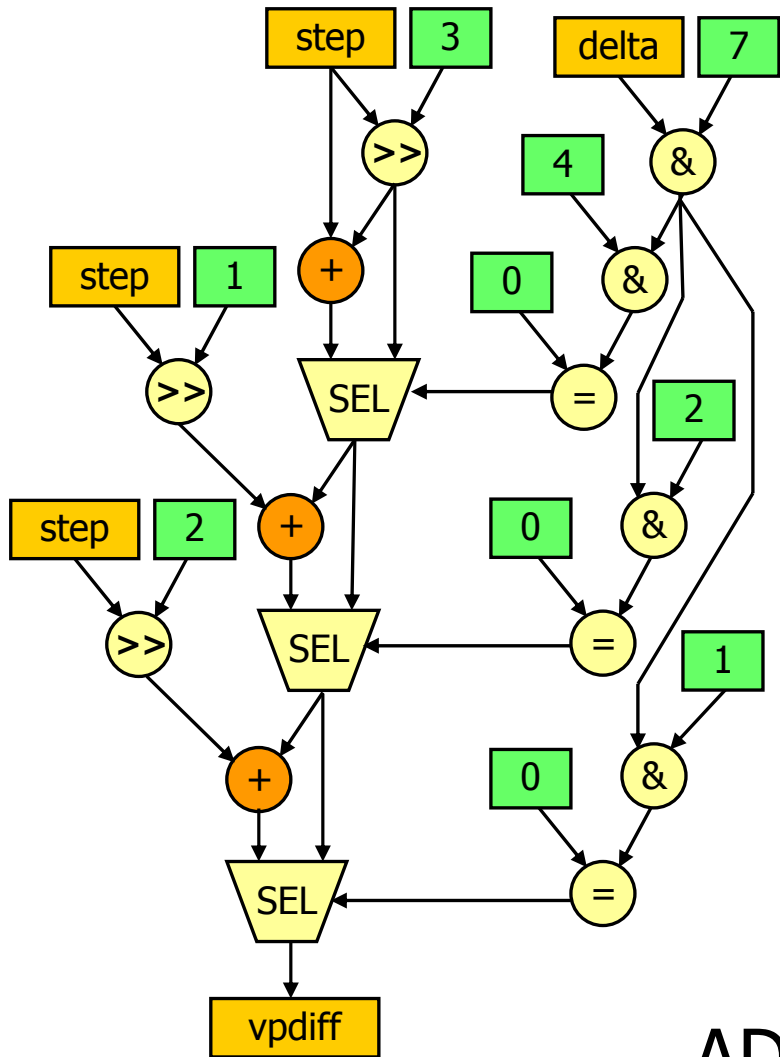

ADPCM January 22, 2008

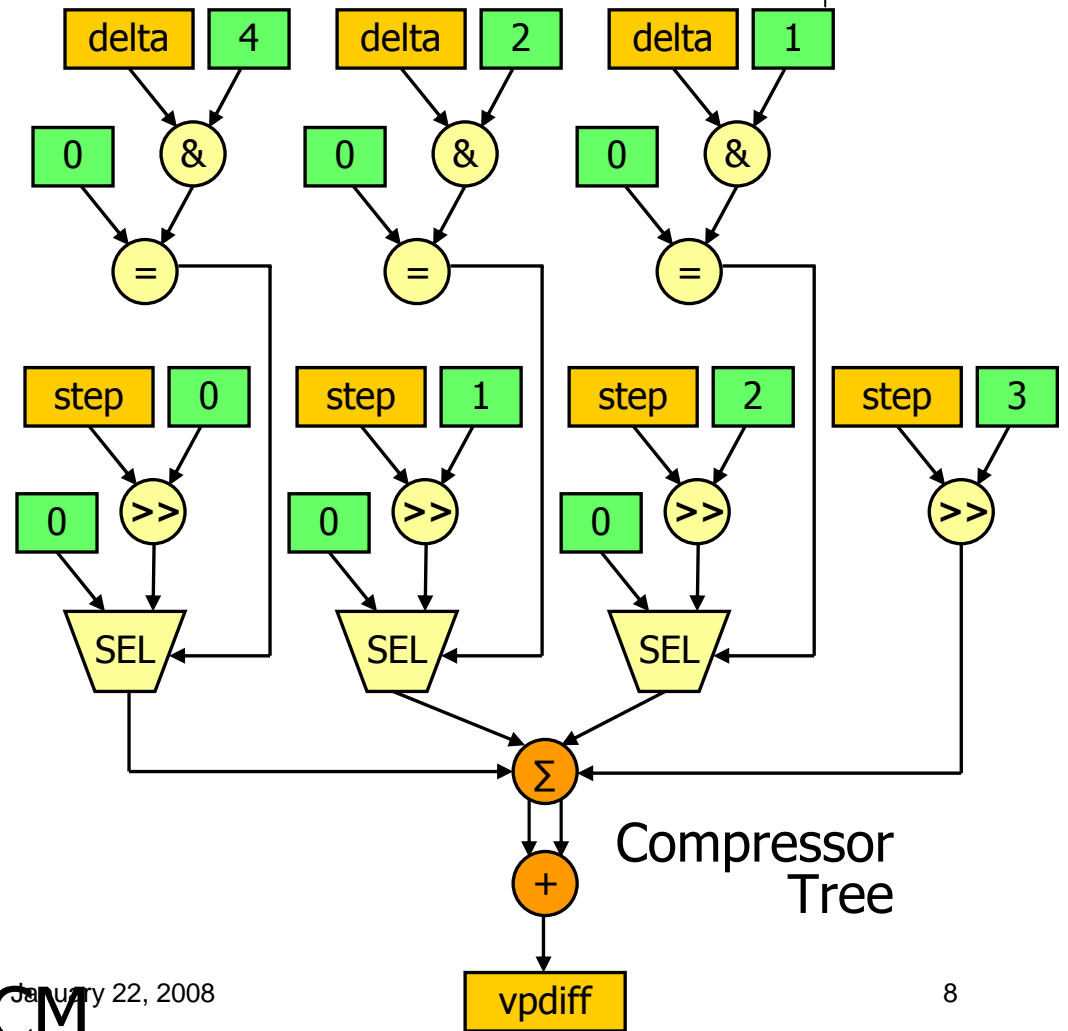



Outline

- State of the Art: FPGAs
- Motivation
- **Generalized Parallel Counters**
- Mapping Heuristic
- Experimental Results
- Conclusion



Counters


Count #of Input Bits Set to 1
Output # as a Binary Value

Counters You Know

2:2 – Half Adder

3:2 – Full Adder

(Carry-Save Adder)

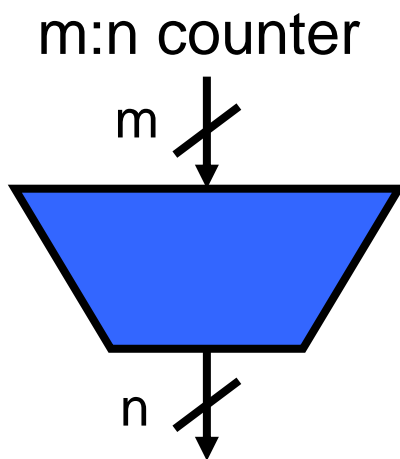

$$n = \lceil \log_2(m+1) \rceil$$

The correct building block for
computing sums of $k > 2$ numbers

Better than LUTs!

Generalized Parallel Counters (GPCs)



- A counter that can sum bits having different ranks
- *Representation:*

$$(K_{N-2}, K_{N-1}, \dots, K_0; S)$$


- IO Constraints: M and N are input and output constraints

$$\sum_{i=0}^{N-2} K_i \leq M$$

$$\sum_{i=0}^{N-2} K_i 2^i \leq 2^N - 1$$

- Examples

- (3, 3; 4) GPC
- (5, 5; 4) GPC

 



GPC Implementation

- Using basic gates
- Using an $m:n$ counter can implement a GPC by connecting all input bits of rank i to $2i$ inputs of the counter
- Using k -LUTs for a k -input GPCs
 - Current FPGAs have bigger LUTs
 - i.e. Three 6-LUTs are required for a $M=6$, $N=3$ GPC



Outline

- State of the Art: FPGAs
- Motivation
- Generalized Parallel Counters
- **Mapping Heuristic**
- Experimental Results
- Conclusion



Mapping Heuristic

- How to:
 - Specify GPC configurations
 - Connect GPCs
- Definitions
 - Primitive GPCs (i.e. $(1, 3; 3)$, $(2, 3; 3)$)
 - Covering GPCs (i.e. $(2, 3; 3)$)
 - Compression ratio
 - Unreasonable GPCs (i.e. $(1, 2; 3)$)



Mapping Heuristics

- Algorithm Objective:
 - Reducing logic levels and GPCs
- Algorithm Inputs:
 - M, N: Input/Output constraints
 - K: Number of final adder rows
 - A set of bits to be summed
- Algorithm contains 7 steps




Mapping Heuristics: Steps

- Steps 1, 2, 3 and 7 are executed once
- Steps 4-6 occur inside a loop that generates the compressor tree.
- Steps:
 - Step1: Extracting covering GPCs.
 - Step2: Extracting primitive GPCs.
 - Step3: Sorting GPC w.r.t. compression ratio
 - Step4: Covering columns using above GPCs
 - Step5: Connecting generated GPCs to previously generated GPCs
 - Step6: Generating output bits of generated GPCs
 - Step7: Final addition, if *number* remained rows is less than K.



Mapping Heuristics: Step4

 - Covers all of the columns of the current logic level of the compressor tree with GPCs
- Finding base column: The tallest column
- Forward search
- Backward search
- Example





Outline

- State of the Art: FPGAs
- Motivation
- Generalized Parallel Counters
- Mapping Heuristic
- **Experimental Results**
- Conclusion




Experimental Methodology

- Altera Stratix-II
 - 90nm CMOS Technology
- For Multi-Input Addition Ops
 - ADD – Adder Tree
 - Ternary Adders in Stratix-II
 - 3GD – Compressor Tree
 - 3 input LUTs
 - GPCs – Compressor Tree, $M=6$ and $N=3$
 - 6 input LUTs, 2 in each ALM



Experimental results (Delay)


27% on average GPC is faster than ADD

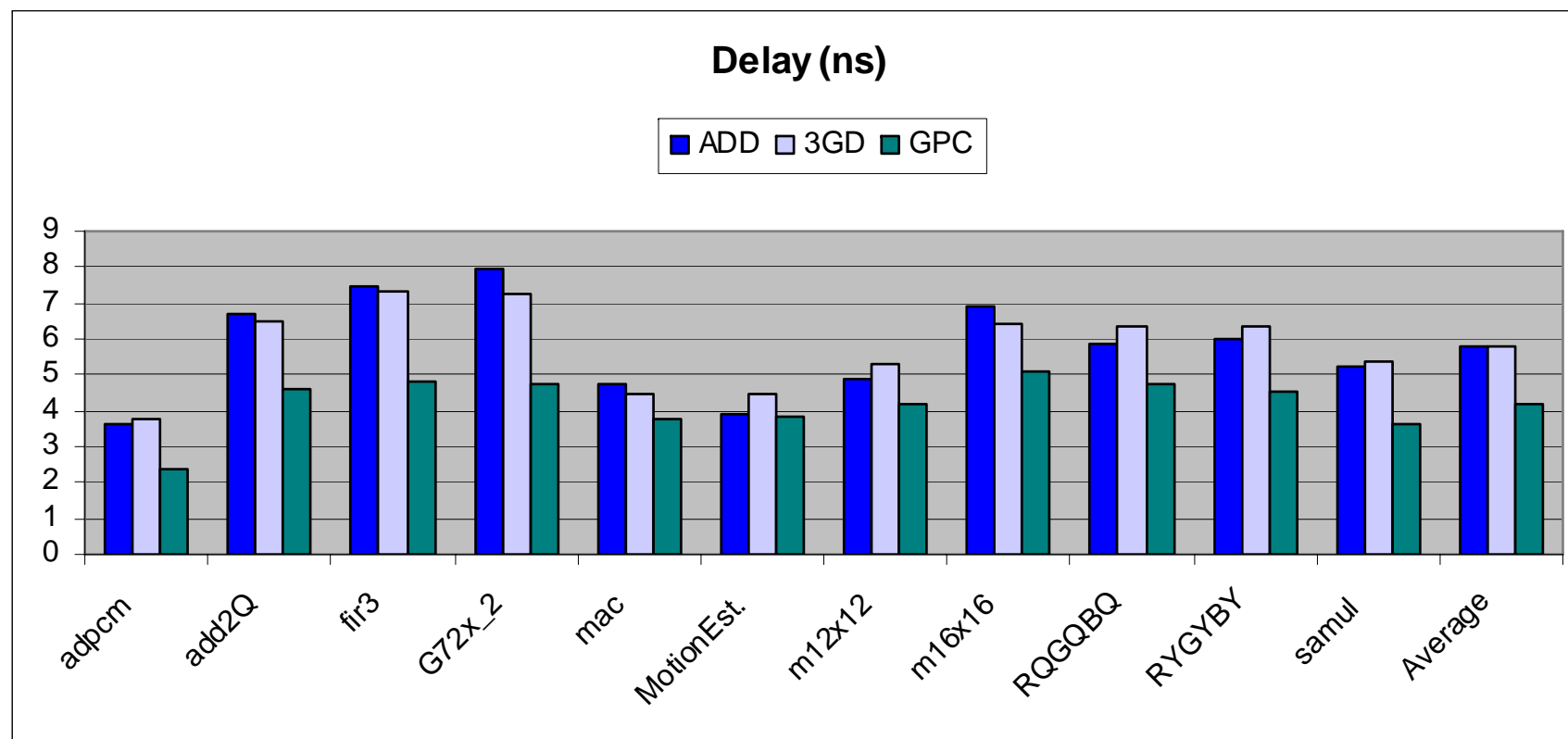




Experimental results (Area)

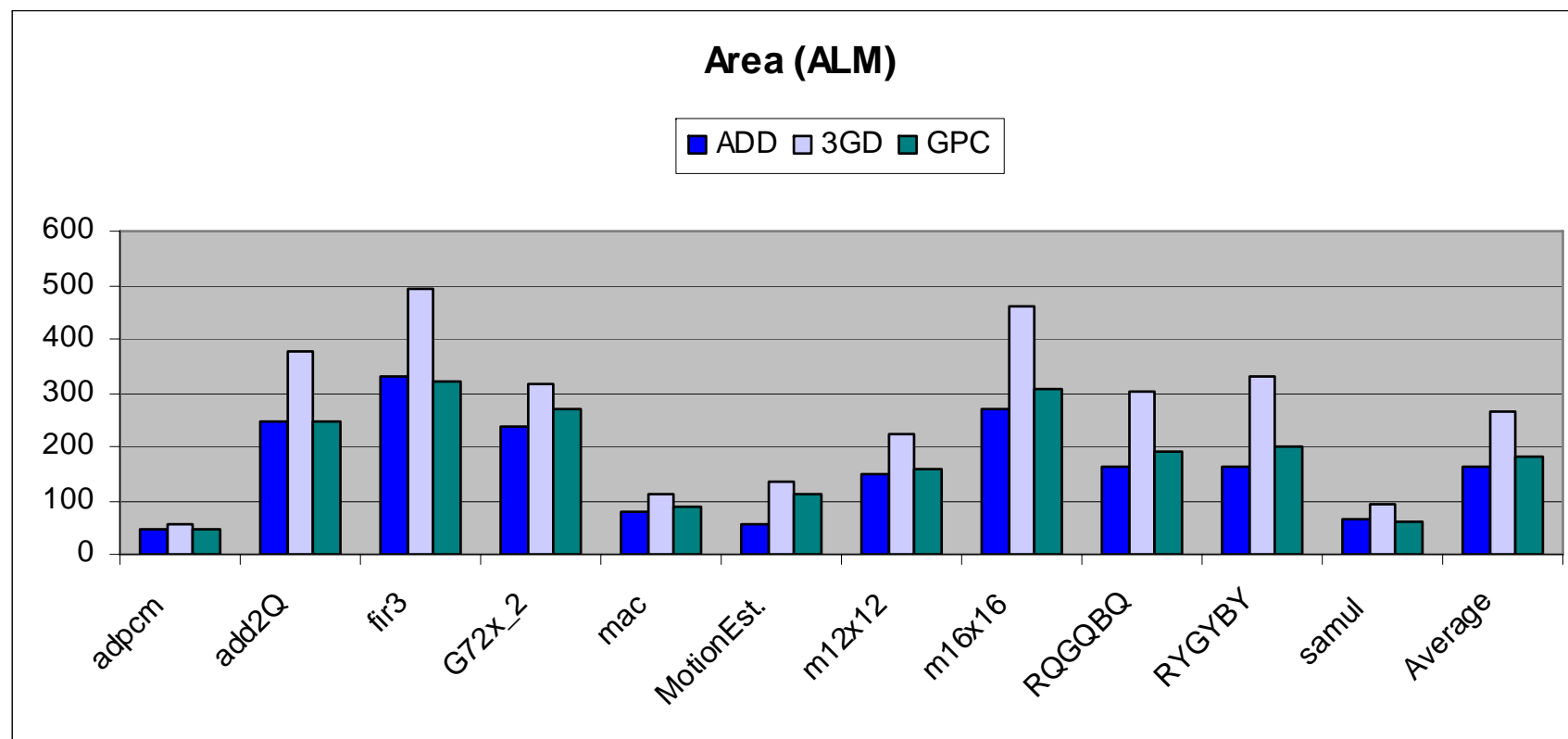5% increase in ALMs usage for GPC compared to ADD



Experimental results (DSPs)

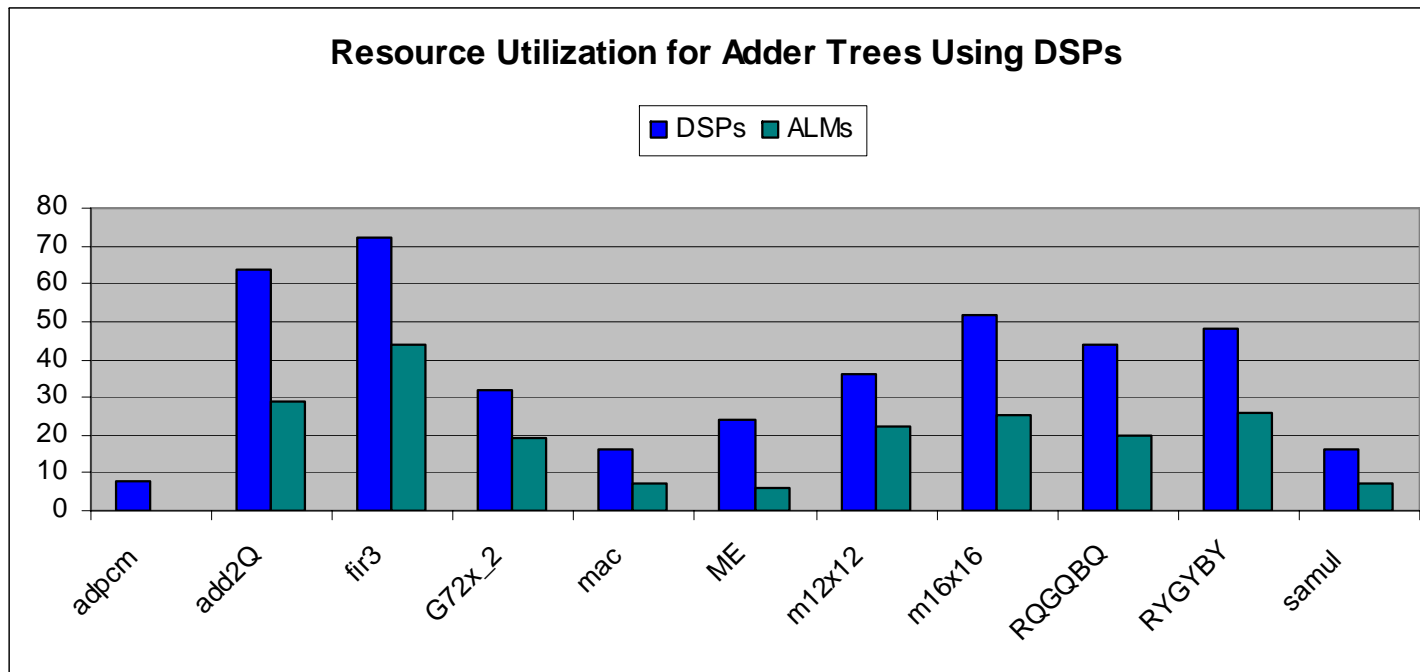



Outline

- State of the Art: FPGAs
- Motivation
- Generalized Parallel Counters
- Mapping Heuristic
- Experimental Results
- **Conclusion**



Conclusion

- GPCs are flexible constructs for mapping compressor trees
- GPCs map to LUTs well
- Compressor trees built from GPCs do map onto FPGAs better than adder trees