

# Method for Multiplier Verification Employing Boolean Equivalence Checking and Arithmetic Bit Level Description

U. Krautz<sup>1</sup>, M. Wedler<sup>1</sup>, W. Kunz<sup>1</sup> &  
K. Weber<sup>2</sup>, C. Jacobi<sup>2</sup>, M. Pflanz<sup>2</sup>

<sup>1</sup>University of Kaiserslautern - Germany

<sup>2</sup>IBM Forschung und Entwicklungs GmbH - Germany

13th Asia and South Pacific Design Automation Conference,  
2008

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 Our Methodology
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 Our Methodology
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

# General Arithmetic Circuit Verification

- formal property checking of significant importance
- arithmetic circuits still “show stoppers”
- no universal framework for arithmetics, instead special “engineered” solutions
- useful for highly regular designs
- limited in case of full custom logic designs
- multipliers particular hard to verify
  - hardware multipliers common in processors
  - hard to generate compact canonical representation from bit level
  - for verification often equivalence check against reference (reference and design have to share large structural similarities)

# General Arithmetic Circuit Verification

- formal property checking of significant importance
- arithmetic circuits still “show stoppers”
- no universal framework for arithmetics, instead special “engineered” solutions
- useful for highly regular designs
- limited in case of full custom logic designs
- multipliers particular hard to verify
  - hardware multipliers common in processors
  - hard to generate compact canonical representation from bit level
  - for verification often equivalence check against reference (reference and design have to share large structural similarities)

# General Arithmetic Circuit Verification

- formal property checking of significant importance
- arithmetic circuits still “show stoppers”
- no universal framework for arithmetics, instead special “engineered” solutions
- useful for highly regular designs
- limited in case of full custom logic designs
- multipliers particular hard to verify
  - hardware multipliers common in processors
  - hard to generate compact canonical representation from bit level
  - for verification often equivalence check against reference (reference and design have to share large structural similarities)



# General Arithmetic Circuit Verification

- formal property checking of significant importance
- arithmetic circuits still “show stoppers”
- no universal framework for arithmetics, instead special “engineered” solutions
- useful for highly regular designs
- limited in case of full custom logic designs
- multipliers particular hard to verify
  - hardware multipliers common in processors
  - hard to generate compact canonical representation from bit level
  - for verification often equivalence check against reference (reference and design have to share large structural similarities)

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 Our Methodology
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

## Previous Work

- Binary Moment Diagrams (\*BMD) [Bryant, Cheng, Hamaguchi]
  - lack of robustness
- functional decomposition [Chang, Cheng, Fujita, Chen, Aagaard, Seger, Kaivola, Narasimhan]
  - prove internal properties
  - compose global proof of sub-goals
  - manual decomposition
  - non-trivial mapping of lowest proof level to design
- comparison of reference and design based on 1bit-adder network [Stoffel, Wedler]
  - extraction of adder network from design and reference (exponential number of possibilities)
  - equivalence proven by simple calculus

## Previous Work

- Binary Moment Diagrams (\*BMD) [Bryant, Cheng, Hamaguchi]
  - lack of robustness
- functional decomposition [Chang, Cheng, Fujita, Chen, Aagaard, Seger, Kaivola, Narasimhan]
  - prove internal properties
  - compose global proof of sub-goals
  - manual decomposition
  - non-trivial mapping of lowest proof level to design
- comparison of reference and design based on 1bit-adder network [Stoffel, Wedler]
  - extraction of adder network from design and reference (exponential number of possibilities)
  - equivalence proven by simple calculus

## Previous Work

- Binary Moment Diagrams (\*BMD) [Bryant, Cheng, Hamaguchi]
  - lack of robustness
- functional decomposition [Chang, Cheng, Fujita, Chen, Aagaard, Seger, Kaivola, Narasimhan]
  - prove internal properties
  - compose global proof of sub-goals
  - manual decomposition
  - non-trivial mapping of lowest proof level to design
- comparison of reference and design based on 1bit-adder network [Stoffel, Wedler]
  - extraction of adder network from design and reference (exponential number of possibilities)
  - equivalence proven by simple calculus

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 Our Methodology
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results


# A Simple Multiplier

## Algorithm

- integer multiplication  
 $((a_0, \dots, a_n) \cdot (b_0, \dots, b_m) = p)$
- basic multiplication (grade school algorithm):

$$\left. \begin{array}{r}
 (a_0, \dots, a_n) \cdot 2^0 \cdot b_0 \\
 + (a_0, \dots, a_n) \cdot 2^1 \cdot b_1 \\
 \vdots \\
 + (a_0, \dots, a_n) \cdot 2^{m-1} \cdot b_{m-1} \\
 + (a_0, \dots, a_n) \cdot 2^m \cdot b_m
 \end{array} \right\}$$

## Structure

 

# Full Custom Multipliers

- custom multipliers @IBM developed on bit-level
- various optimizations
  - no half-adder instances (just “AND”, “XOR”-gates)
  - full-adders spread across cycles
  - no booth-encoder instances (just shifter, multiplexer)
  - constant bits in adder-tree
  - hot-one/ hot-two representation
- no word level information available (hard to extract)



# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 **Our Methodology**
  - Excursion: Multiplier Design
  - **ARDL**
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

# Arithmetic Reference Description Language

- utilized in verification
- specify multiplier on word level:
  - arithmetic by functions
  - structure by interconnection between functions
- syntax close to HD languages (Verilog / VHDL)
  - used by designer, not verification engineer
- developed at beginning of design process
  - formalization of typical considerations before implementing a design

## ARDL Extract - 3Bit Radix2 Multiplier Example


```

variables {
a: in (0 to 2);
b: in (0 to 2);
...}
pp_def{
ppb(0) <= gen_pp(a(0 to 2), booth22(0 & 0 & b(0)));
ppb(1) <= gen_pp(a(0 to 2), booth22(b( 0 to 2)));
...}
tree_def{
s1a <= sum32 (ppb(0), ppb(1), ppb(2));
c1a <= carry32 (ppb(0), ppb(1), ppb(2));
sum <= s1a;
carry <= c1a
...}
    
```

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 **Our Methodology**
  - Excursion: Multiplier Design
  - ARDL
  - **Overview**
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results


# Approach Overview

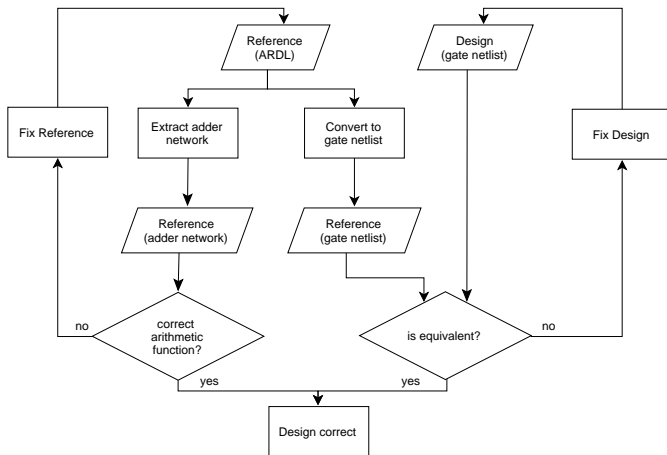

# Outline


- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 **Our Methodology**
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - **Arithmetic Proof**
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

# Overview Arithmetic Proof

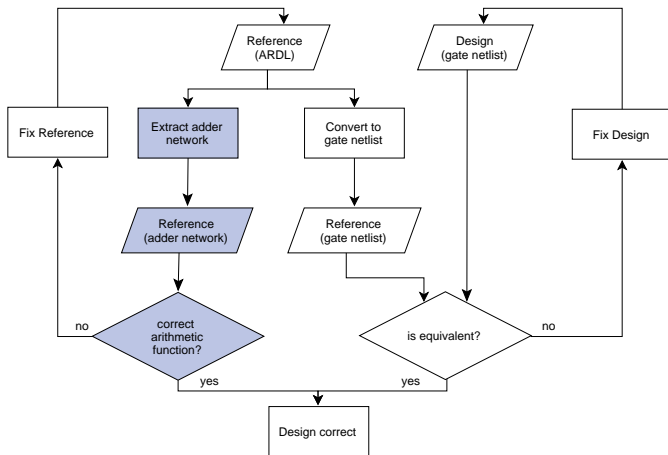

# ARDL to Structure

## structural view

 

- input: ARDL of multiplier design (given by designer)

## functional view

$$a = (a_0, \dots, a_n),$$

$$b = (b_0, \dots, b_m)$$

$$pp_j = a \cdot B_j,$$

$$B_j = -2ab_{j+1} + ab_j + ab_{j-1}$$

$$prod = \sum_{j=0}^m pp_j$$

- arithm. functions derived from ARDL structure (automatically)
  - Booth encoding
  - adder network



# Structure to Bit Arithmetic

## functional view

$$a = (a_0, \dots, a_n),$$

$$b = (b_0, \dots, b_m)$$

$$pp_j = a \cdot B_j,$$

$$B_j = -2ab_{j+1} + ab_j + ab_{j-1}$$

$$prod = \sum_{j=0}^m pp_j$$

- arithm. functions derived from ARDL structure (automatically)
  - Booth encoding
  - adder network

## bit arithmetic

0	0	0	$-2a_0b_2$
0	$a_0b_1$	$a_1b_1$	$a_2b_1$
$a_1b_0$	$a_0b_2$	$a_1b_2$	$a_2b_2$

- transformation to basic multiplier definition (automatically)
  - successful/unsuccessful  $\rightarrow$  correct/incorrect arithmetic

# Example Booth encoded 3bit multiplier

initial situation

0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	$-2a_0b_2$	$-2a_1b_2$	$-2a_2b_2$
0	0	$a_0b_1$	$a_1b_1$	$a_2b_1$	0	0
0	0	$a_0b_2$	$a_1b_2$	$a_2b_2$	0	0
0	0	$-2a_0b_0$	$-2a_1b_0$	$-2a_2b_0$	0	0
$a_0b_0$	$a_1b_0$	$a_2b_0$	0	0	0	0
0	0	0	0	0	0	0
$p_{-1}$	$p_0$	$p_1$	$p_2$	$p_3$	$p_4$	

# Example Booth encoded 3bit multiplier

after transformation

0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	$-a_0 b_2$	$-a_1 b_2$	$-a_2 b_2$	0
0	0	$a_0 b_1$	$a_1 b_1$	$a_2 b_1$	0	0
0	0	0	$2a_0 b_2$	$2a_1 b_2$	$2a_2 b_2$	0
0	$-a_0 b_0$	$-a_1 b_0$	$-a_2 b_0$	0	0	0
0	$2a_0 b_0$	$2a_1 b_0$	$2a_2 b_0$	0	0	0
0	0	0	0	0	0	0
$p_{-1}$	$p_0$	$p_1$	$p_2$	$p_3$	$p_4$	

# Example Booth encoded 3bit multiplier


after summation

0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	$a_0 b_1$	$a_1 b_1$	$a_2 b_1$	0	0
0	0	0	$a_0 b_2$	$a_1 b_2$	$a_2 b_2$	0
0	0	0	0	0	0	0
0	$a_0 b_0$	$a_1 b_0$	$a_2 b_0$	0	0	0
0	0	0	0	0	0	0
$p_{-1}$	$p_0$	$p_1$	$p_2$	$p_3$	$p_4$	

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 **Our Methodology**
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - **Equivalence Check**
- 3 Our Results/Contribution
  - Main Results


# Overview - Equivalence Check

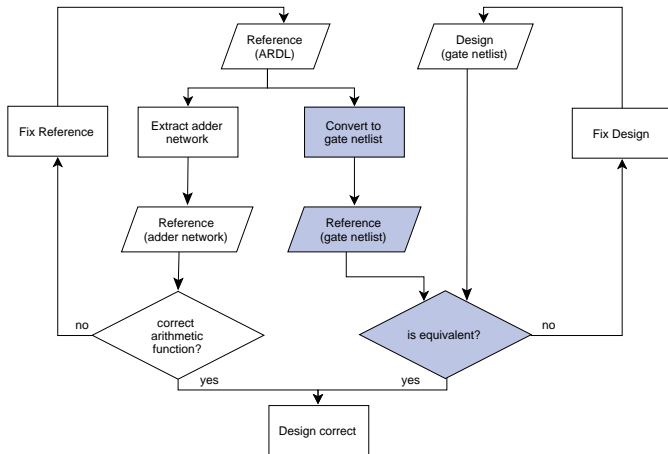

## Equivalence Check

- ARDL structure translated into gate-list reference
- functions synthesized into pre-defined blocks (Booth-encoder, adder,...)
- equivalence checked of reference against design (standard SAT solver)
- successful check requires similarities between reference and design
  - similar inputs to adder-tree (same Booth-encoding)
  - adder-tree topology
  - assignments to adders (order of inputs)
- similarities through design concept in ARDL
  - similarities result through methodology
  - designer's responsibility

# Overview - Final

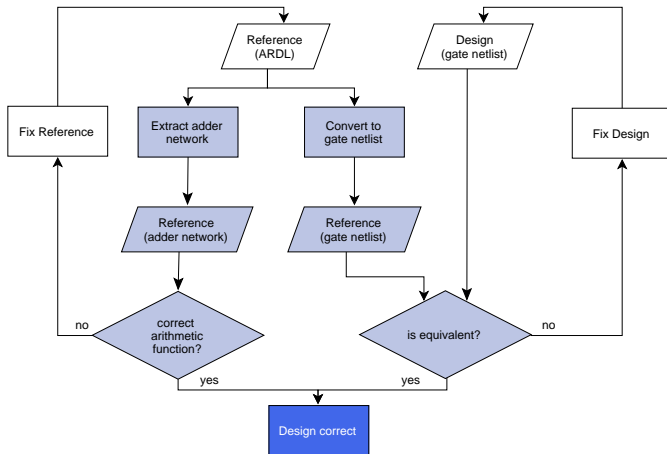



## Scope of Method

- arithmetic circuits modeled at word-level, with easy to derive bit-level
  - data-path verification
  - arithmetic otherwise hard to obtain from gate netlist
  - flexible
- multicycle operations through unrolling

# Outline

- 1 Motivation
  - The Basic Problem
  - Other Approaches
- 2 Our Methodology
  - Excursion: Multiplier Design
  - ARDL
  - Overview
  - Arithmetic Proof
  - Equivalence Check
- 3 Our Results/Contribution
  - Main Results

# Implementation/ Experiments

- prototype implementation (PERL)
- used on several industrial multipliers (IBM)
- complex instructions
  - parallel operations in wide multipliers
  - require different ARDL for each instruction

Operation (operand's bit width)	cpu time	
	AP	EC
4x4	0.6s	2s
8x8	1s	2s
8x8+8x8+8x8+8x8	9s	2s
16x16+16x16	9s	10s
24x24	7s	10s
53x53	8min	15s
64x64	14min	21s

## Conclusion

- ARDL suited for binary multiplier designs (FPU, FXU, ...)
- manual effort negligible (formalization of typical design considerations)
- applied to complex instructions (multiply-add)
- unsigned, signed multiplication possible

# Summary

- Verification method for multipliers:
- special **reference description in ARDL** (Arithmetic Reference Description Language)
- ARDL reference for **simple bit arithmetic check** - transformation to basic multiplication
- ARDL reference for **construction of gate-list representation** - equivalence check against design

Thank you

Questions?