



A Current-based Method for Short Circuit Power Calculation Under Noisy Input Waveforms

Hanif Fatemi, Shahin Nazarian, Massoud Pedram
University of Southern California
Los Angeles, CA

Asia and South Pacific Design Automation


Jan 26th, 2007

Outline

- **Motivation**
- **Introduction**
- **Current Source Modeling**
- **A Current-based Short-circuit Power Calculator**
- **Experimental Results**
- **Conclusion**

Power Analysis

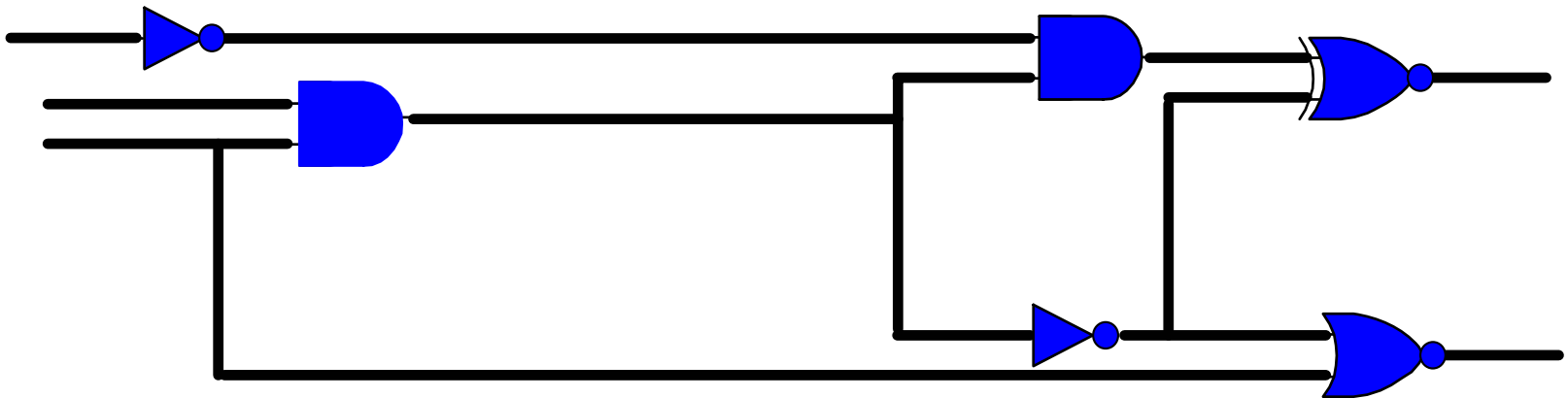- A digital CMOS circuit is a collection of CMOS gates:




- Accurate power estimation is a critical step in the analysis and design of such circuits


Power Analysis Challenges

- **Input pattern dependency:**
 - Knowledge of a “typical” or “expected” input stream
 - E.g., Signal probability, switching activity, spatio-temporal correlation
 - Addressed by various statistical and/or probabilistic power estimation techniques
- **Variability in the shape of the input signal waveform**
 - Due to different sources of noise, such as crosstalk noise and DC drop on supply lines and /or process variation

Sources of Power Consumption in CMOS

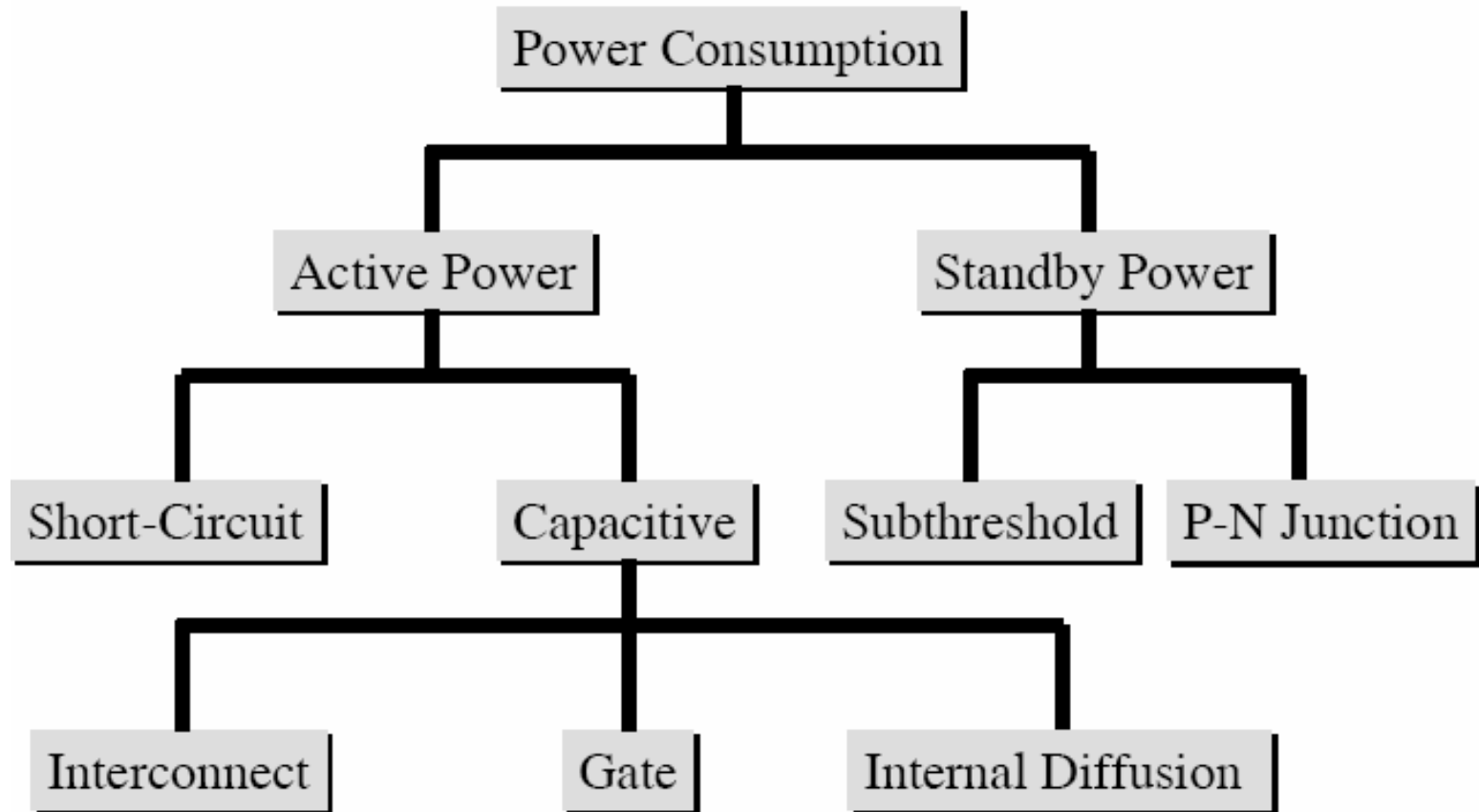

Short Circuit Power Calculation

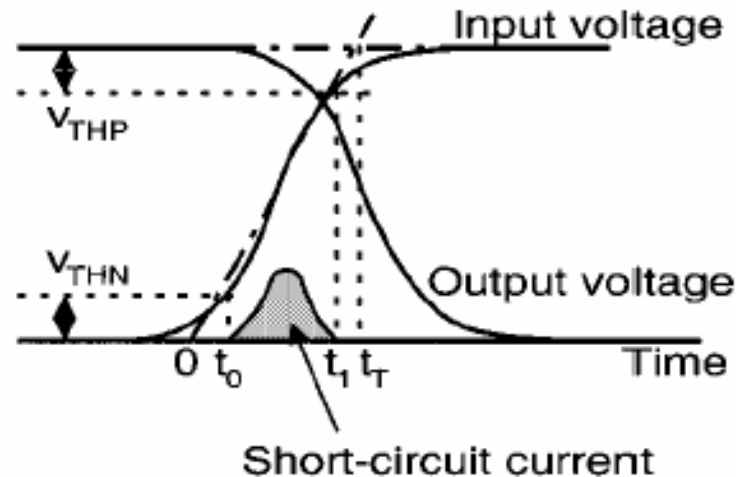

- **Short circuit current:**
 - Due to current the flows from the Vdd rail to ground during an output transition
 - Depends on the duration of time that transistors in the pull-up and pull-down sections of a CMOS logic cell operate in each region of the transistor operation
 - Depends on both input and output voltage waveforms
- **How to measure short circuit current and energy dissipation?**

Prior Work

- **Closed-form analytical expressions based on simple device models:**
 - H. Veendrick (1984), based on the Shichman–Hodges model
 - S. Vemuri et al. (1994) and K. Nose et al. (2000) based on the alpha-power model
 - L. Rossello et al. (2002) based on a charge-based device model called MM9
 - Lack of accuracy due to use of simple device models and assumptions made regarding the device operation during signal transitions
- **Pre-characterization:**
 - Dartu et al. (1996), based on input signal transition time and capacitive output load
- **Generalized device equations and table lookup based computations**
 - Acar et al. (2003), quadrilateral model of short circuit current waveform
- **All these techniques assume a ramp signal as the input**


Short Circuit Power Calculation Flow

- **Problem statement:**

Develop a short circuit power calculator capable of handling noisy inputs (including glitches) with arbitrary shapes


- **Solution:**

**Utilize Current-
purpose of SC**

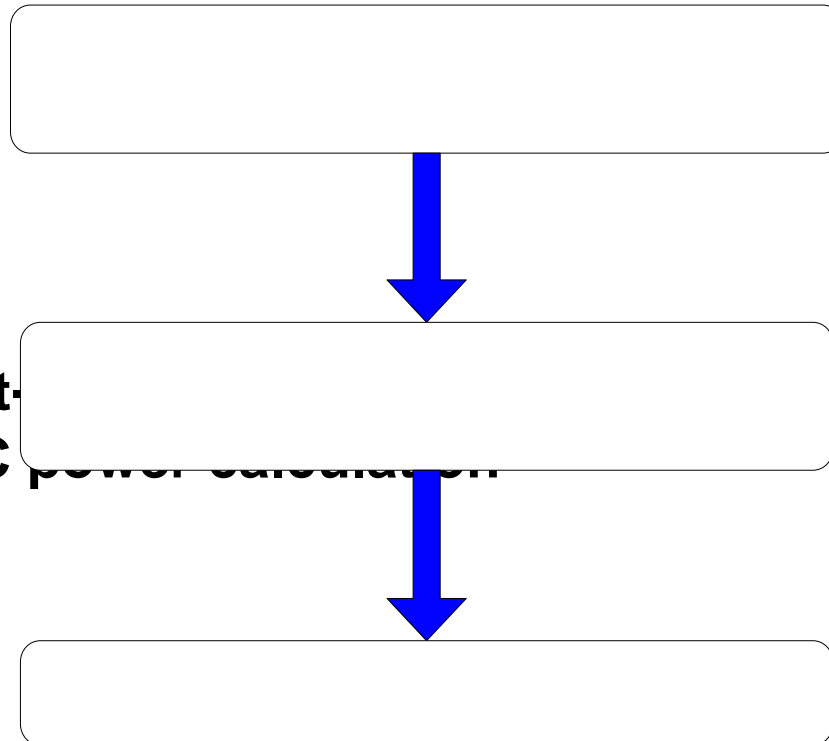

logic cells for the

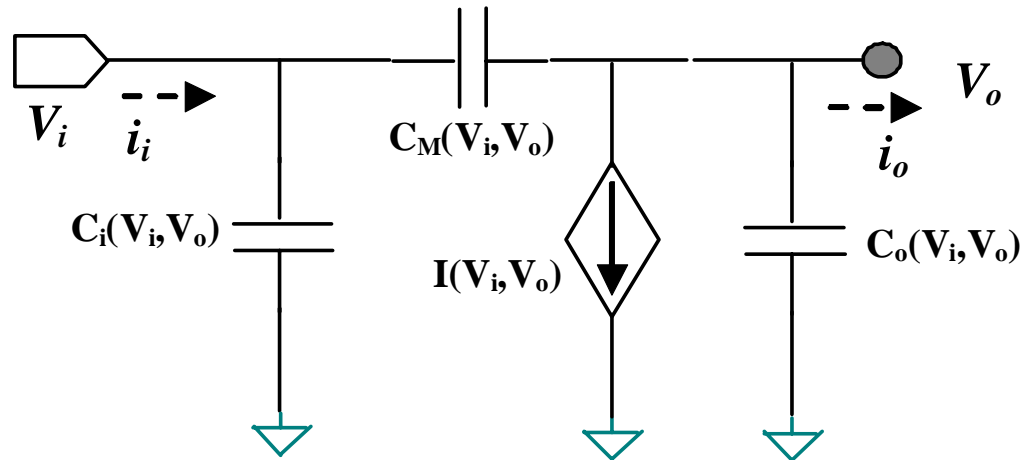
Our Current Source Model (Fatemi et al. DAC 06)



$$i_o + C_o \frac{\Delta V_o}{\Delta t} + I(V_i, V_o) + C_M \frac{\Delta V_o}{\Delta t} - C_M \frac{\Delta V_i}{\Delta t} = 0$$

- **The non-linear behavior of the logic cell:**
 - 2-D lookup table to store $I(V_i, V_o)$
- **Parasitic effects in the logic cell:**
 - 2-D lookup tables to store $C_i(V_i, V_o)$, $C_M(V_i, V_o)$, and $C_o(V_i, V_o)$
- **Series of SPICE simulations to pre-characterize various elements of the CSM model**

CSM Pre-characterization: Current Source

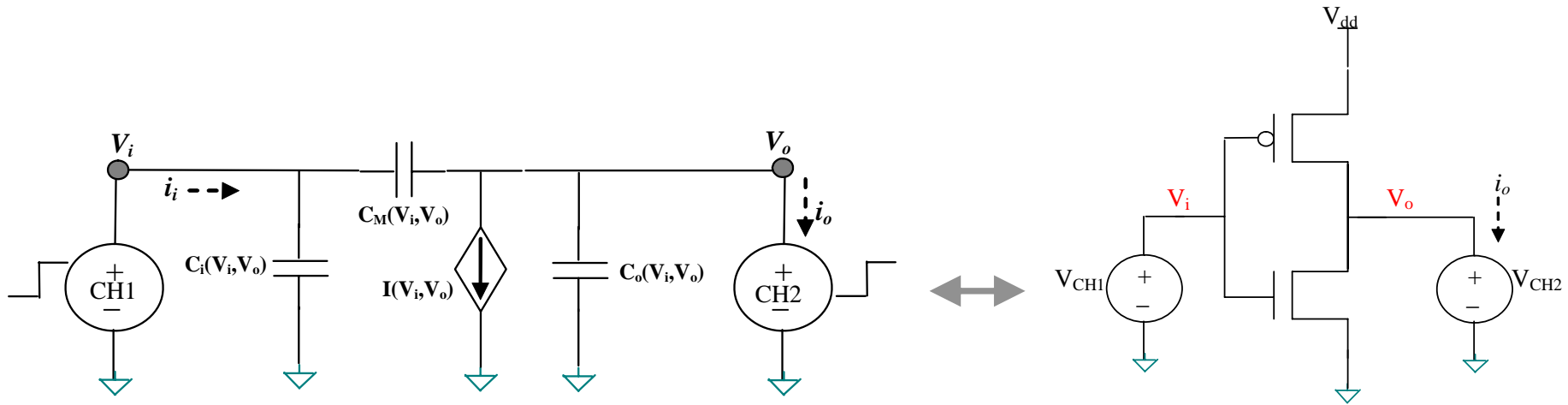


$$i_o + C_o \frac{\Delta V_o}{\Delta t} + I(V_i, V_o) + C_M \frac{\Delta V_o}{\Delta t} - C_M \frac{\Delta V_i}{\Delta t} = 0$$

- $I(V_i, V_o)$:

- Apply DC voltage sources V_{CH1} and V_{CH2} to the input and output
- Measure i_o (the current going through V_{CH2}) in SPICE and fill the entry $I(V_{CH1}, V_{CH2})$ of the table
- Sweep the DC voltage sources

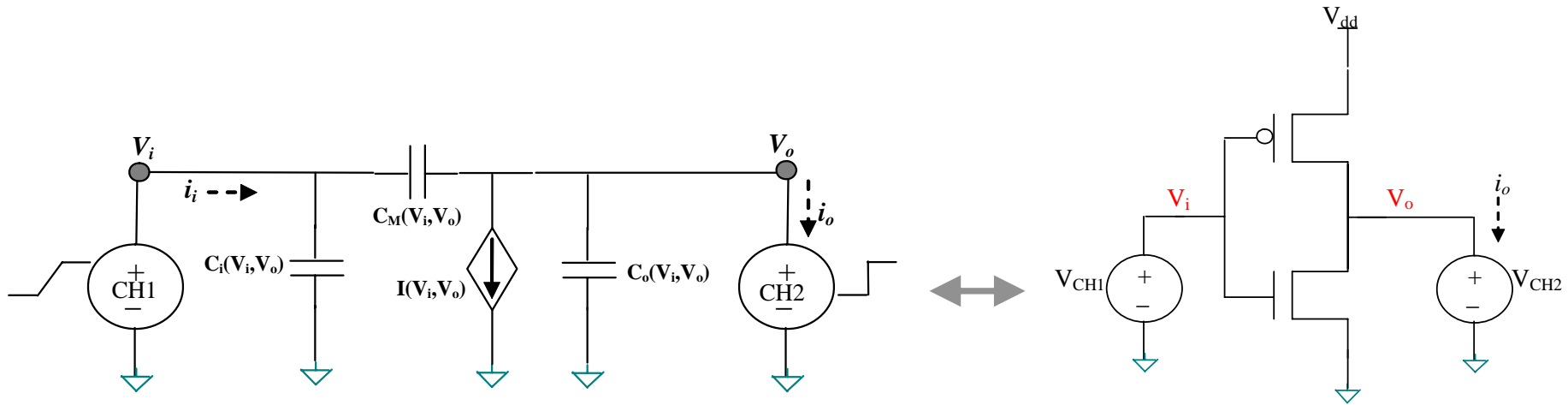
CSM Pre-characterization: Parasitics (C_M)



$$i_o + \cancel{C_o \frac{\Delta V_o}{\Delta t}} + I(V_i, V_o) + \cancel{C_M \frac{\Delta V_o}{\Delta t}} - C_M \frac{\Delta V_i}{\Delta t} = 0$$

- $C_M(V_i, V_o)$
 - Apply a ramp voltage source to input and a DC source to output
 - Measure i_o in SPICE for different voltage values at the input
 - Calculate C_M from the KCL eqn and fill out one column of the table
 - Sweep the DC voltage source at the output

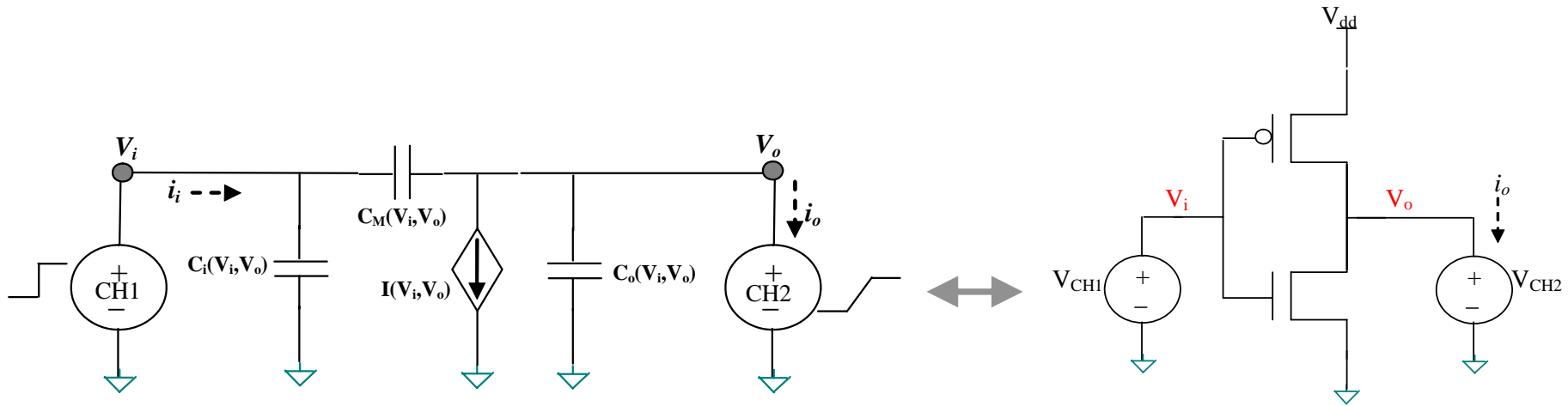
CSM Pre-characterization: Parasitics (C_o)



$$i_o + C_o \frac{\Delta V_o}{\Delta t} + I(V_i, V_o) + C_M \frac{\Delta V_o}{\Delta t} - \cancel{C_M \frac{\Delta V_i}{\Delta t}} = 0$$

- $C_o(V_i, V_o)$
 - Apply a DC source to input and a ramp voltage source to output
 - Measure i_o in SPICE for different voltage values at the output
 - Calculate C_o from the KCL eqn and fill out one row of the table
 - Sweep the DC voltage source at the input

Voltage Calculation Using CSM

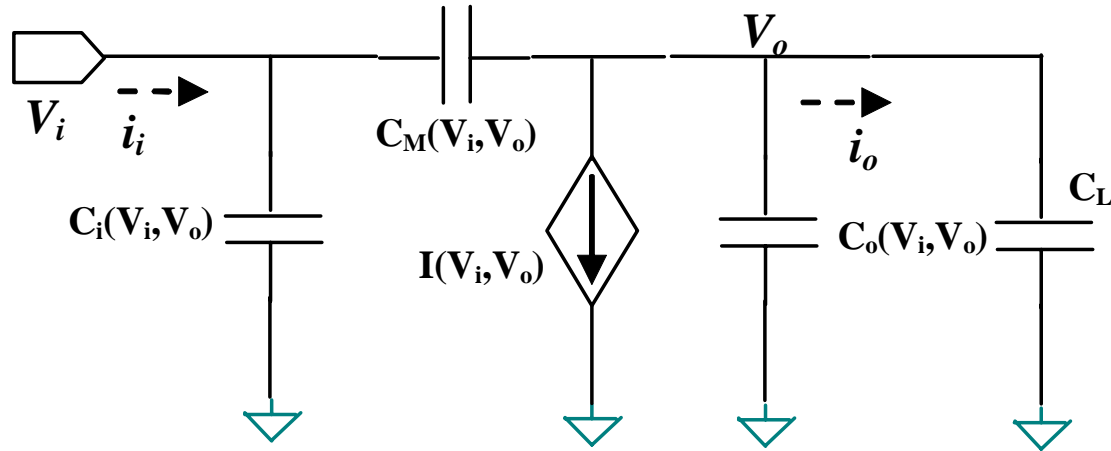


$$C_L \frac{\Delta V_o}{\Delta t} + C_o \frac{\Delta V_o}{\Delta t} + I(V_i, V_o) + C_M \frac{\Delta V_o}{\Delta t} - C_M \frac{\Delta V_i}{\Delta t} = 0$$

$V_o(t_{k+1})$: Calculated based on $V_o(t_k)$ and $V_i(t_k)$, $V_i(t_{k+1})$ and the current source and parasitic capacitance values

$$V_o(t_{k+1}) = V_o(t_k) + \frac{1}{C_L + C_o + C_M} \cdot \left\{ C_M \cdot (V_i(t_{k+1}) - V_i(t_k)) - I(V_i(t_{k+1}), V_o(t_k)) \cdot \Delta t \right\}$$

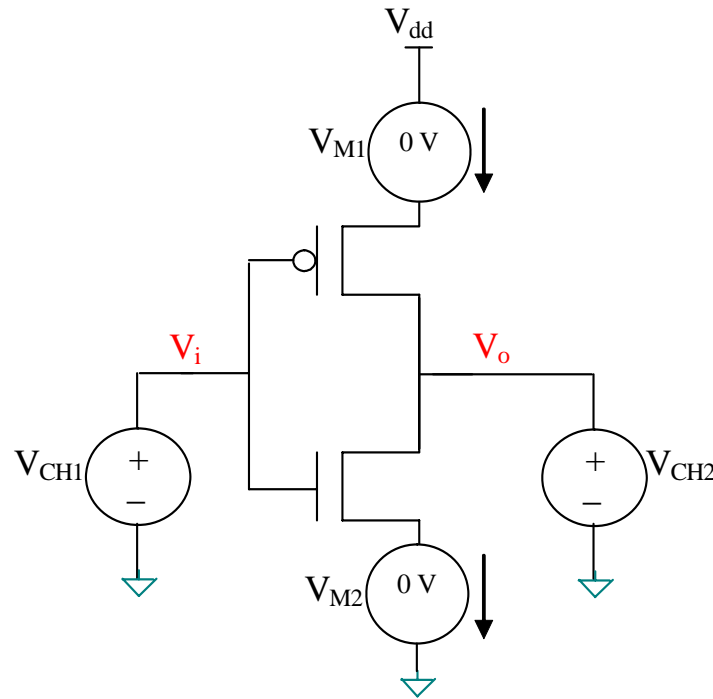Short Circuit Current Pre-characterization




- $I_{sc}(V_{CH1}, V_{CH2}) = \text{Min} \{I(V_{M1}), I(V_{M2})\}$
- A new 2-D lookup table is created to store the $I_{sc}(V_{CH1}, V_{CH2})$ values
- Complexity of the CSM does not increase by the SCC pre-characterization

CSM-based Short Circuit Power Calculator (CSPC)

- **Step 1: Construct the output voltage waveform from on the noisy input waveform by using our CSM-based calculator**
- **Step 2: At each time instance, read the corresponding short circuit current from the look up table and thus construct the exact short circuit (SC) current waveform**
- **Step 3: Report the short circuit energy dissipation associated with the input-output transition as the area under the SC current waveform**

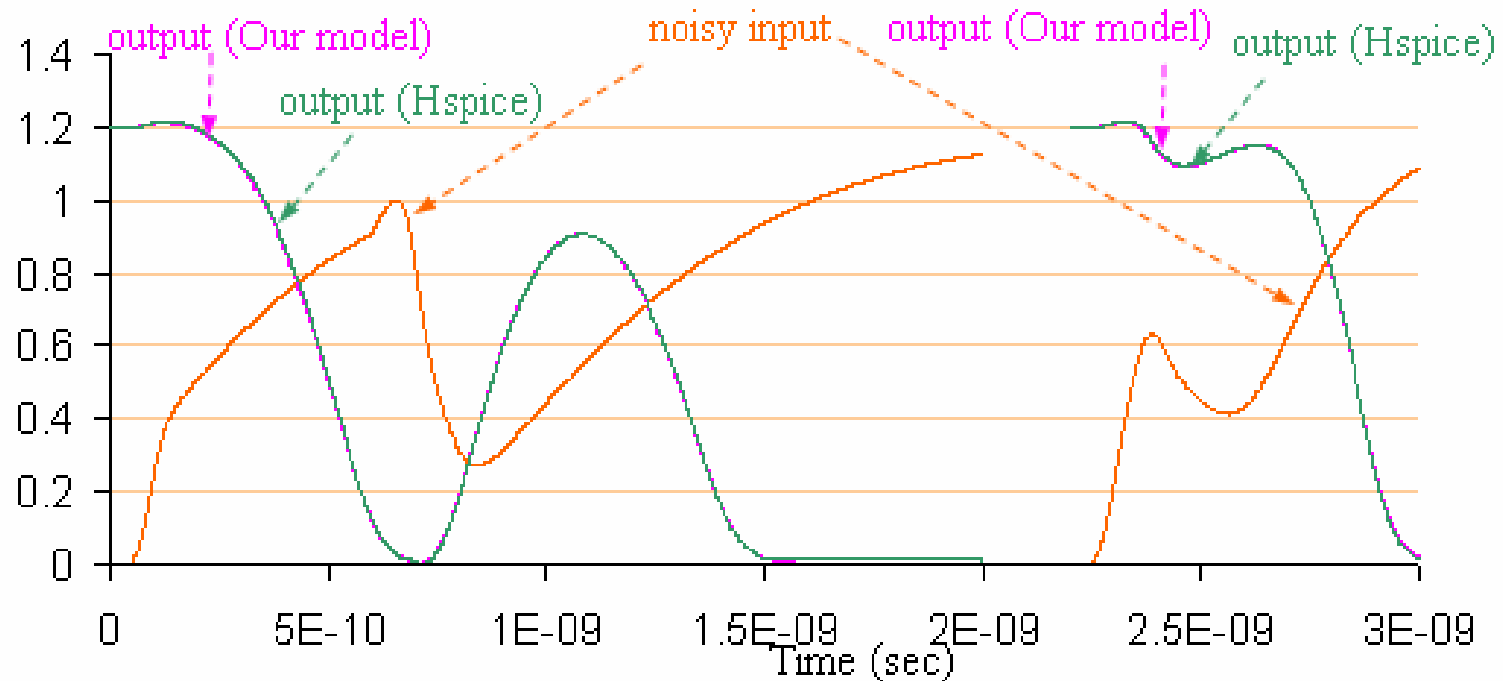
Experimental Results: CSM-based Technique



- **Logic cell: Minimum sized inverter in a 130nm CMOS cell library**
- **HSPICE and our CSM-based calculator results for some (crosstalk-induced) noisy input waveforms**


Experimental Results – Accuracy of CSPC

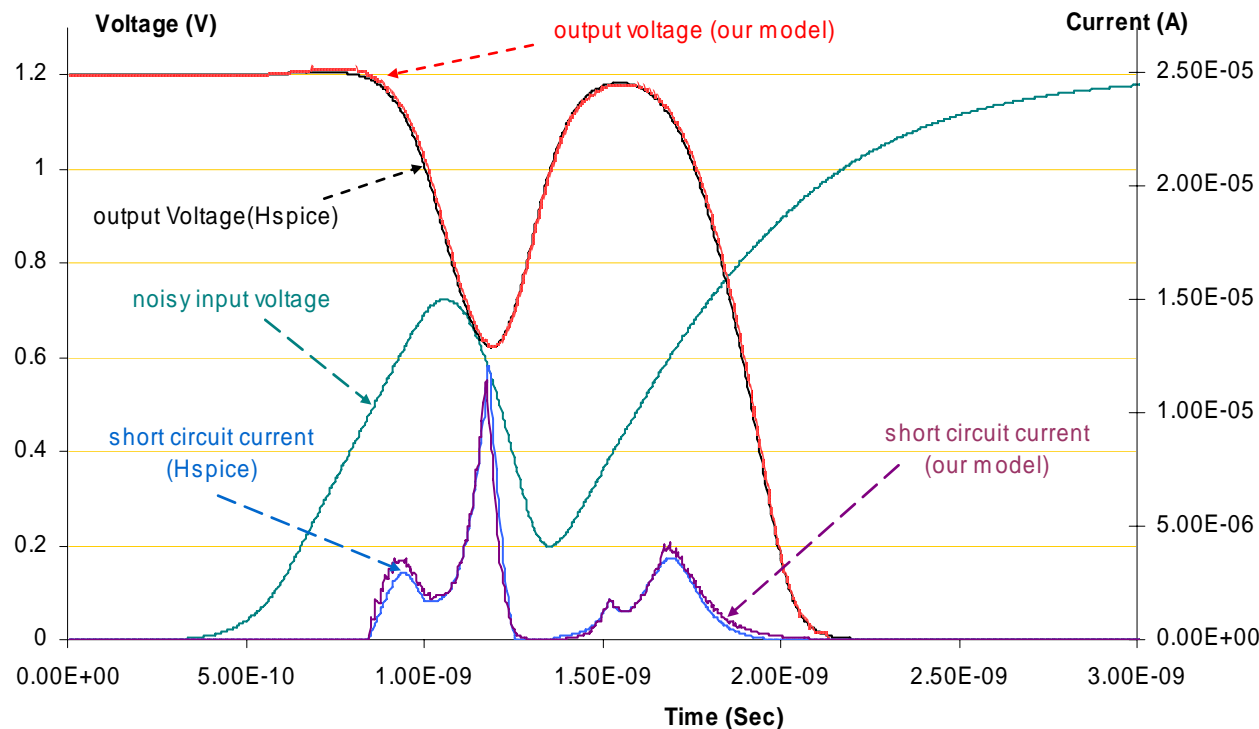- Noisy waveform given to a minimum sized inverter with a FO4 loading in our 130nm cell library
- Switching energy consumption per transition is 8.89fJ
- SC energy dissipation is 2.68fJ (2.78fJ) per Hspice (CSPC)
- E_{sc}/E_{sw} ratio of 30.1%




Comparison with Previous Techniques

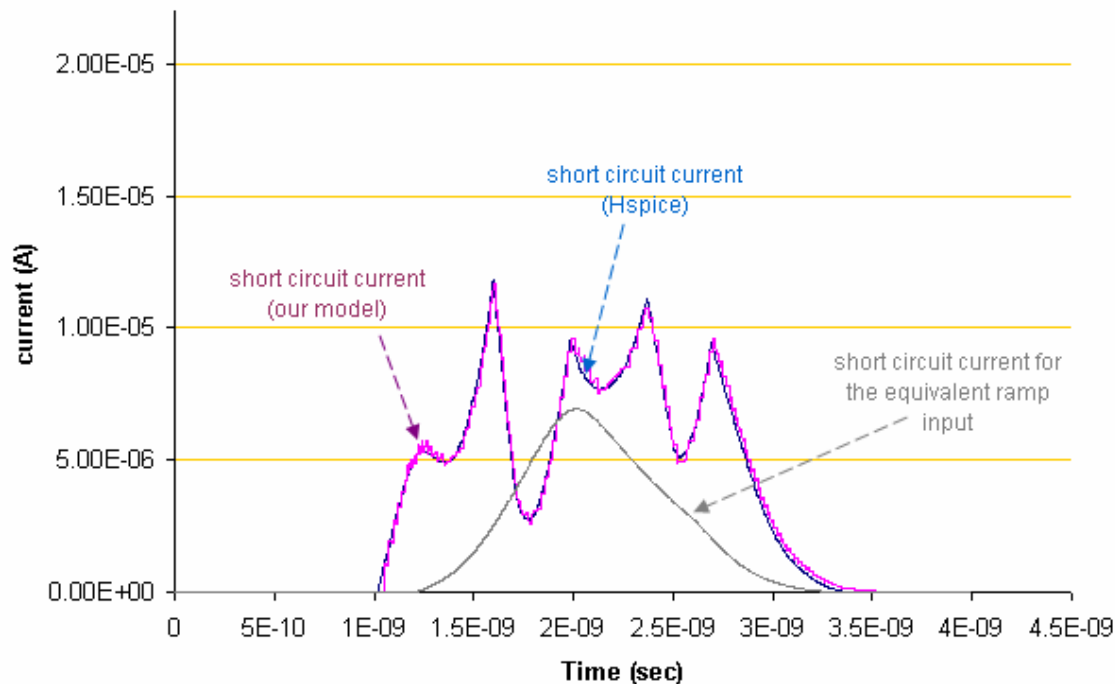- **Saturated ramp approximation of input waveform and use of pre-characterized lookup tables $E_{sc}(t_{in}, C_L)$**
 - SC energy dissipation reported by ramp approximation is 7.1fJ
 - 45.9% error w.r.t. to Hspice short circuit energy report of 15.45fJ
 - SC energy dissipation reported by CSPC is 15.61J (1% error)
 - Shape of the input waveform should not be ignored





Experimental Results – Glitches


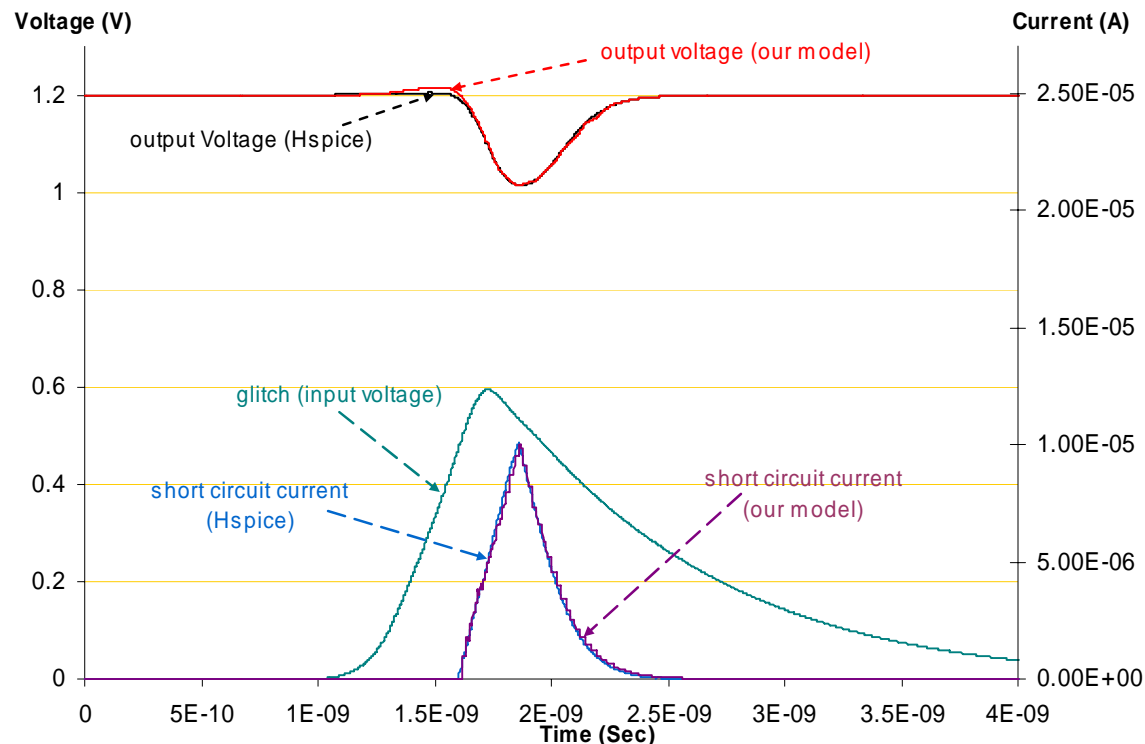
- **Glitches are typically ignored by the timing analysis or a validation tools**
 - **However, the corresponding SC energy dissipation may not be negligible (3.5fJ for the example shown below)**



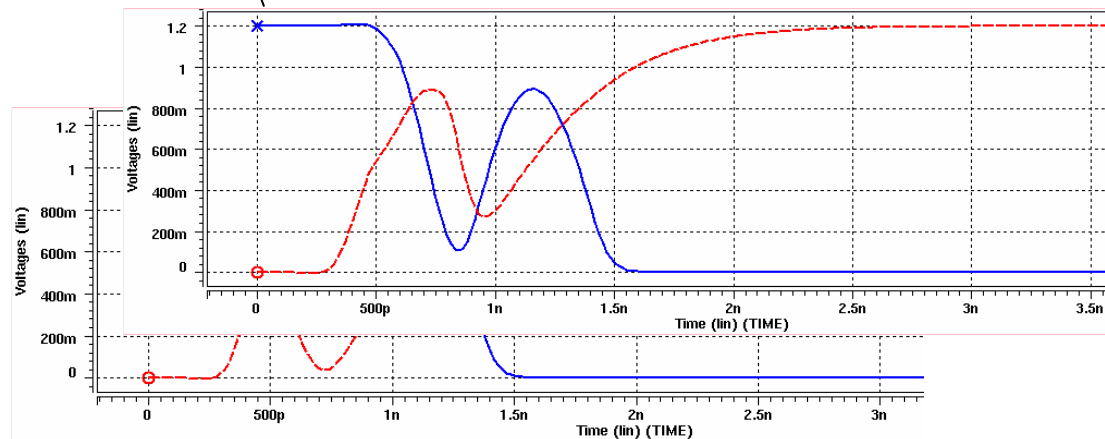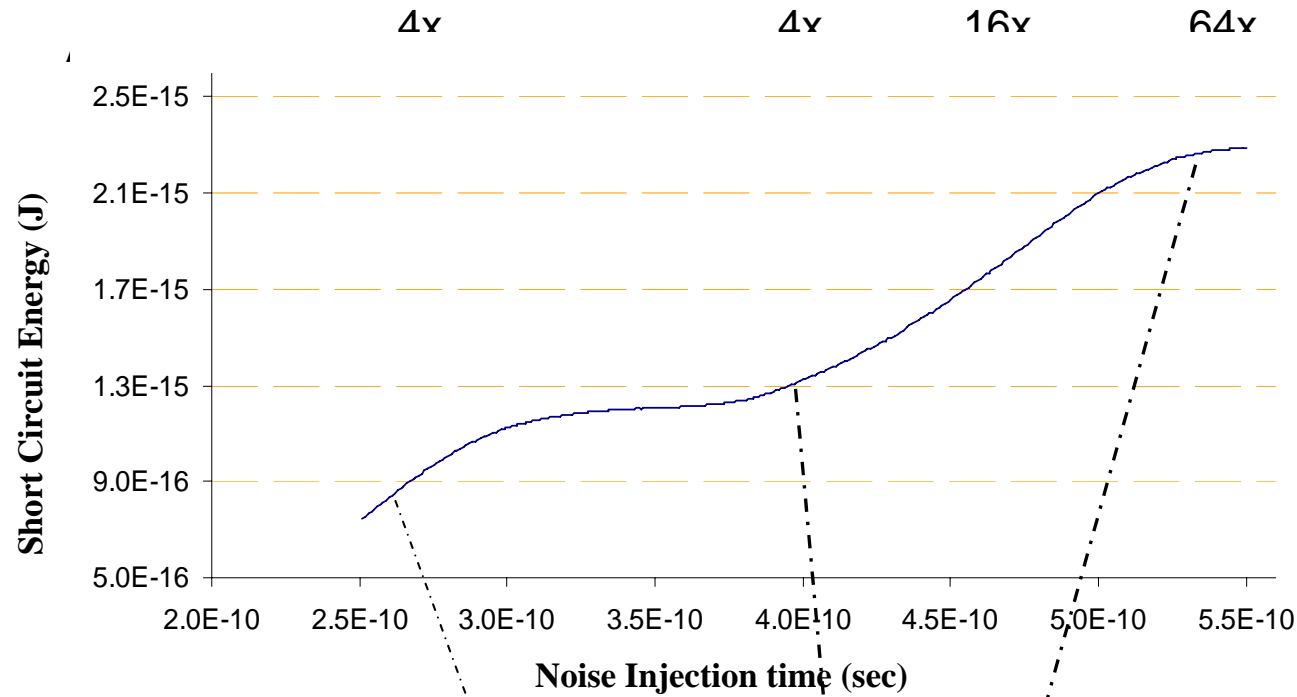Short Circuit Energy in the Presence of Crosstalk



Accuracy and Runtime of CSPC

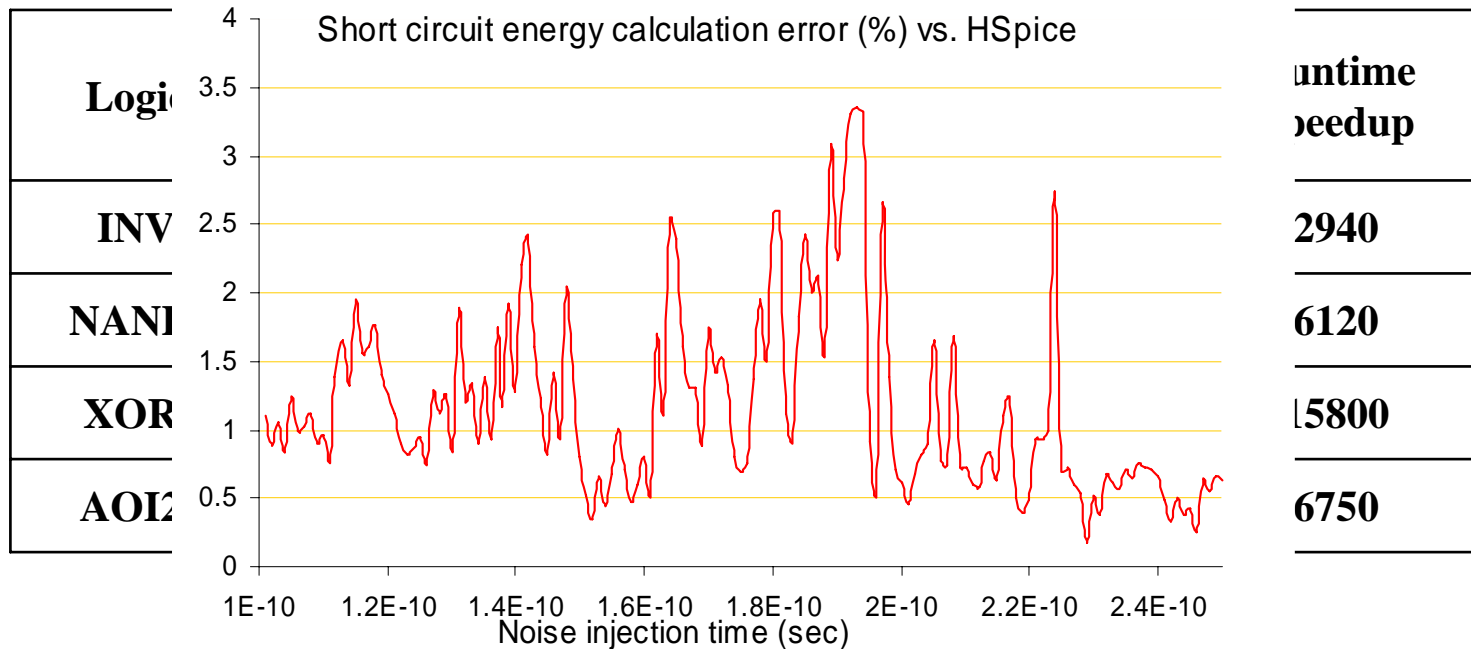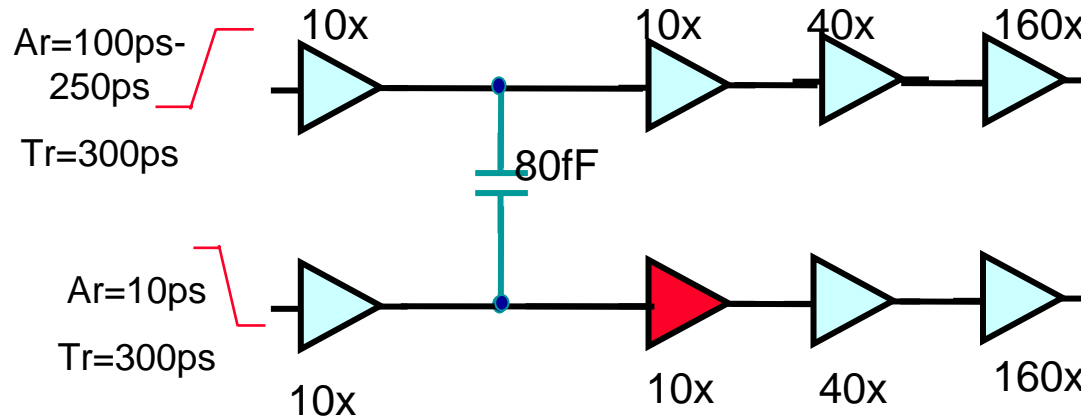

Conclusion

- **Short circuit energy dissipation increases in the presence of noise such as capacitive crosstalk**
- **Previous short circuit calculation methods are not capable of handling noisy input waveforms**
- **We utilize our CSM-based waveform calculator for the purpose of short circuit current calculation**
 - **The output voltage waveform constructed by the CSM-based calculator is used to estimate the short circuit current and hence the corresponding energy dissipation**
 - **Our model is also capable of calculating the short circuit energy consumption of the glitches.**
- **Hpsice-based experimental results prove the high accuracy of our technique**