



# Efficient Synthesis of Quantum Circuits Implementing Clifford Group Operations

**Philipp Niemann, Robert Wille, and Rolf Drechsler**

University of Bremen, Germany




{pniemann,rwille,drechsle}@informatik.uni-bremen.de

# Outline

- Introduction
  - Background and Motivation
  - Synthesis of Quantum Circuits
  - Clifford Group
- Synthesis of Clifford Group Circuits
- Experimental Results and Conclusion

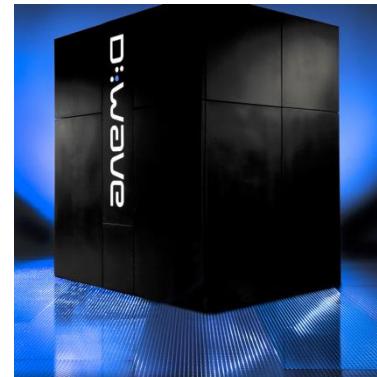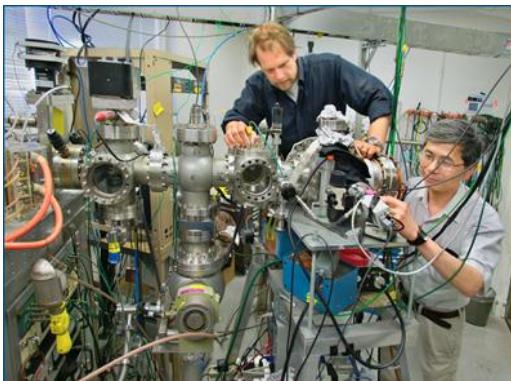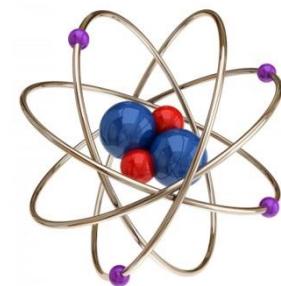
# Motivation

- Conventional techniques (e.g. CMOS) approach atomic border
- Promising alternative: quantum computation
  - exploiting quantum-mechanical phenomena
  - fast algorithms for important problems




# Quantum Computation

- Quantum Bits (*qubits*)
  - basis states  $|0\rangle$  and  $|1\rangle$
  - superposition  $|\Psi\rangle = \alpha|0\rangle + \beta|1\rangle$   $|\alpha|^2 + |\beta|^2 = 1$
- Quantum Circuits

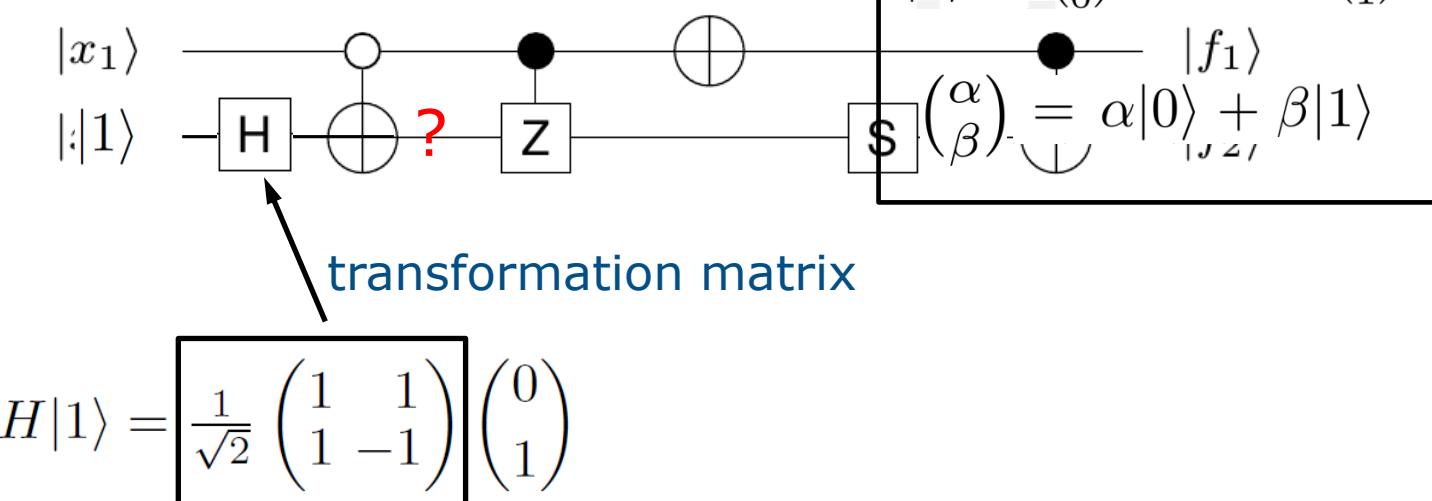
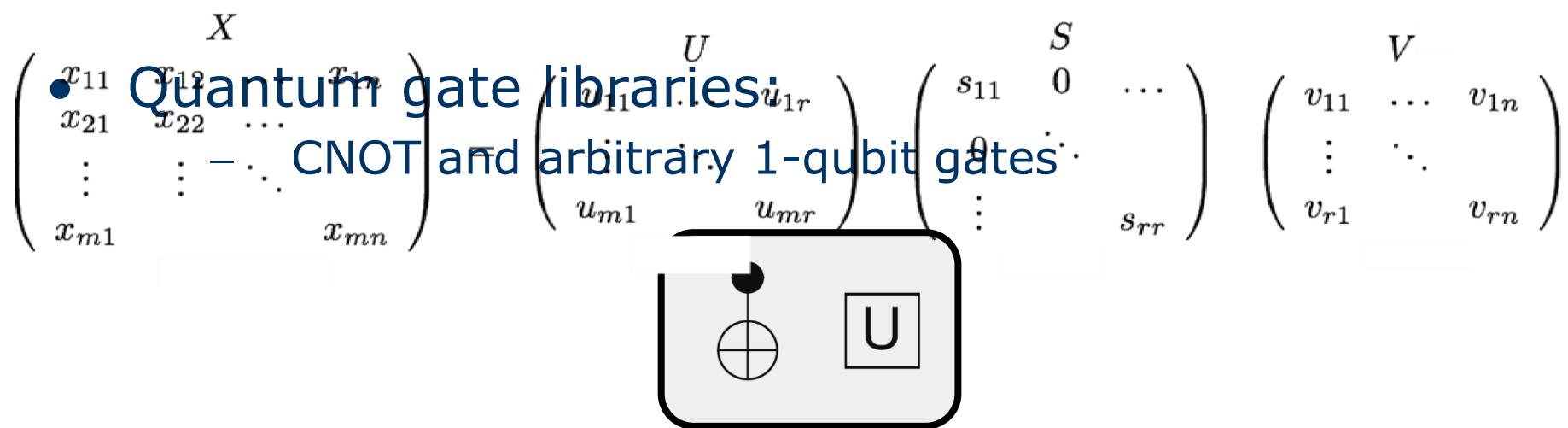
# Synthesis of Quantum Circuits




- Synthesis
  - Decomposition of transformation matrix
  - using only gates from a restricted library



- in practice, gates have to be approximated
- fault tolerance?

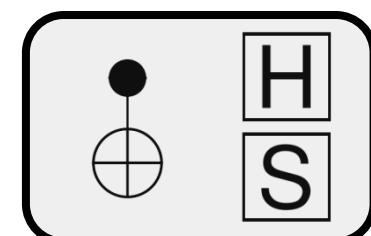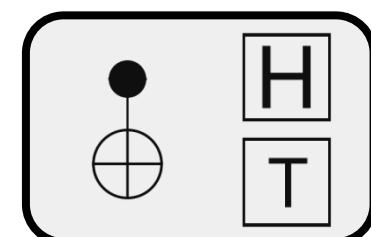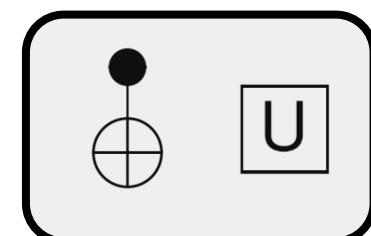
# Quantum Gate Libraries (continued)

- CNOT and arbitrary 1-qubit gates
  - universal, but hard to realize
- CNOT, Hadamard and T gates
  - universal and fault-tolerant
  - approximation overhead
- CNOT, Hadamard and  $S=T^2$  gates
  - *Clifford group*



# Clifford Group Operations

- Gate library

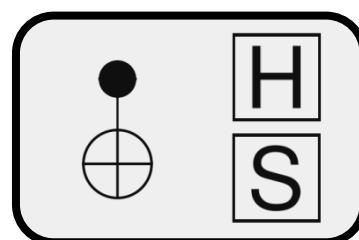

- Cover core aspects of quantum functionality
  - (superposition, entanglement, phase shifts)
- Not universal, but sufficient for many applications
  - error-correcting codes (stabilizer circuits)
  - quantum teleportation
  - dense quantum coding



# Outline

- Introduction
  - Background and Motivation
  - Synthesis of Quantum Circuits
  - Clifford Group
- Synthesis of Clifford Group Circuits
  - Effects on Transformation matrices
  - General idea
  - Running example
- Experimental Results and Conclusion

# Effects on Transformation Matrices




$x_2$	00	01	10	11
$x_1$	00	01	10	11
00	0	0	1	0
01	0	0	0	$-i$
10	$i$	0	0	0
11	0	1	0	0

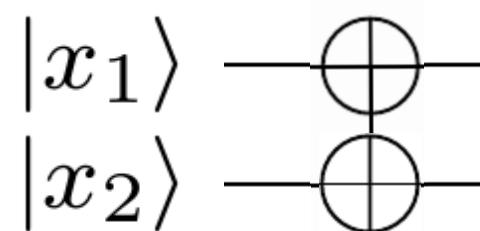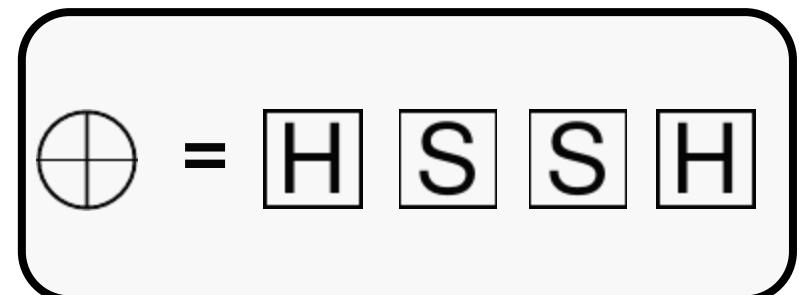

- Permute columns


# Effects on Transformation Matrices

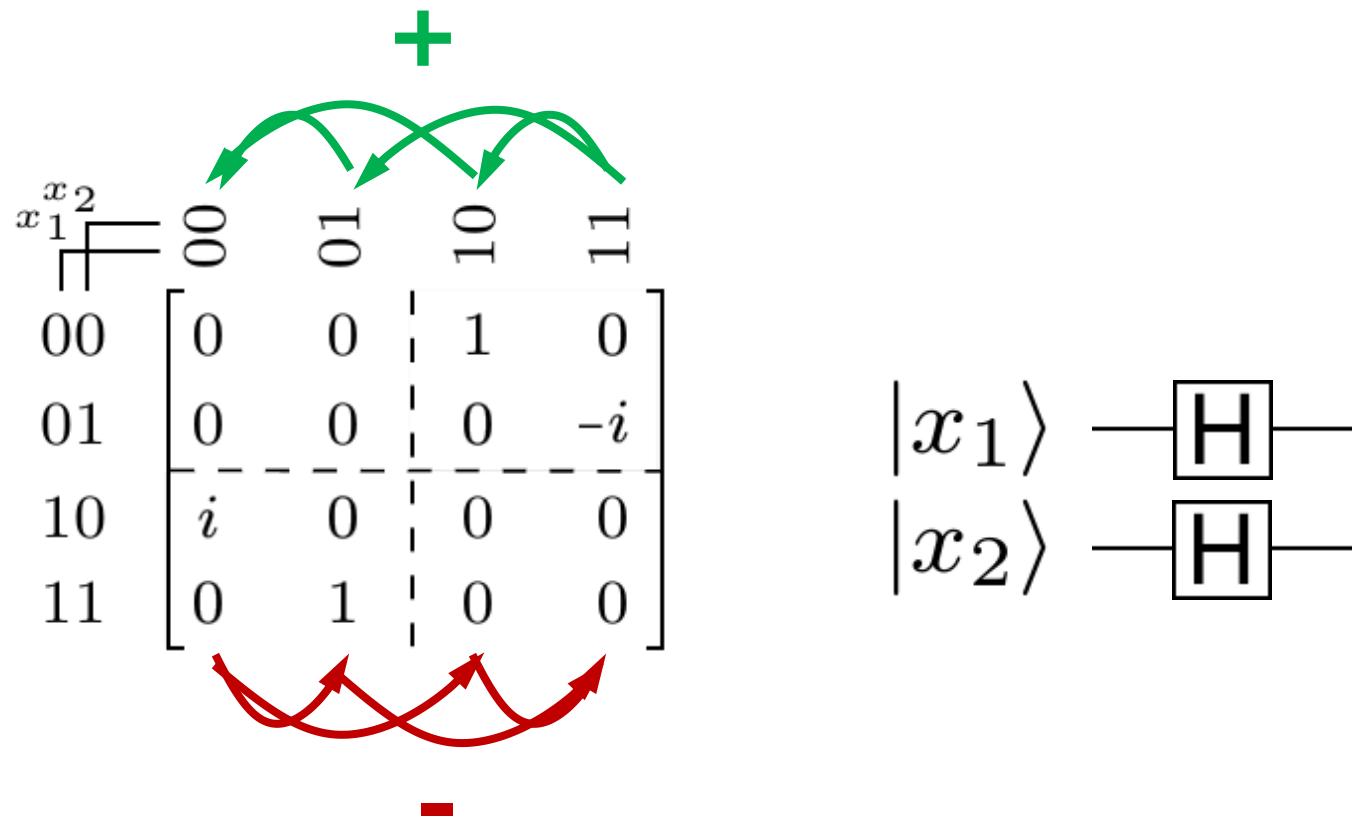



- Combine columns

# Effects on Transformation Matrices

Multiply by -1

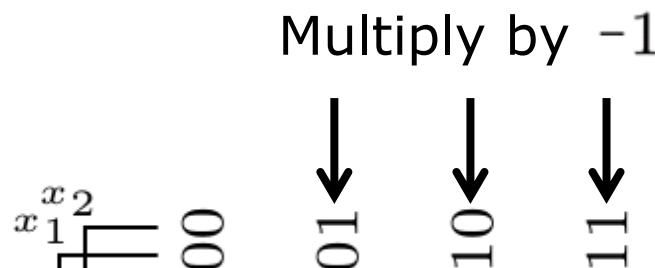



$x_2$	00	01	10	11
00	0 0	1 0		
01	0 0	0 -i		
10	i 0	0 0		
11	0 1	0 0		

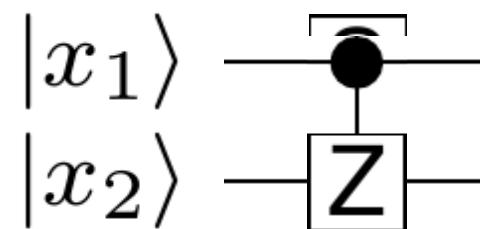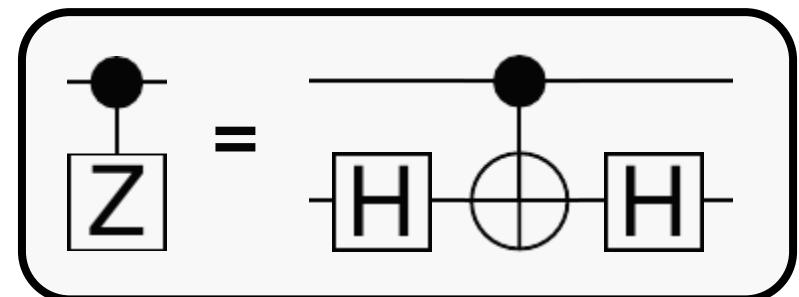

- Modify phase

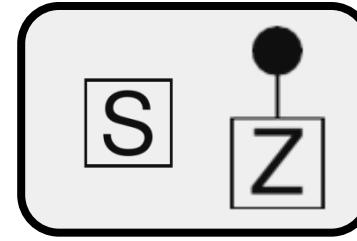
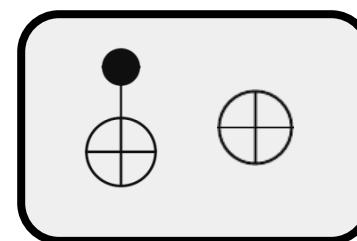
# Effects on Transformation Matrices

- Summary
  - permute columns
  - combine columns
  - modify phase



# Synthesis of Clifford Group Circuits

- General Idea

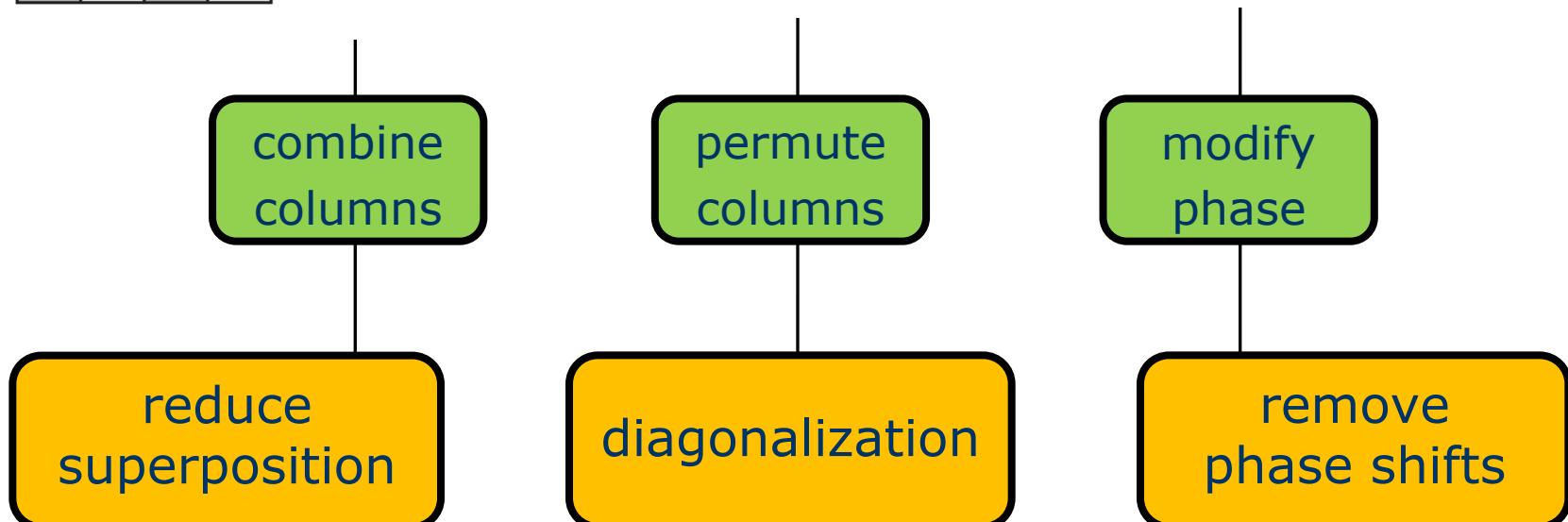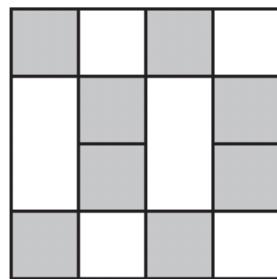

# Running example (Step 1)

$x_2$	000	001	010	011	100	101	110	111
$x_1$	0	$\frac{1}{2}$	0	$\frac{1}{2}$	0	$\frac{i}{2}$	0	$\frac{-i}{2}$
$x_0$	0	0	$\frac{1}{2}$	0	$\frac{-i}{2}$	0	$\frac{i}{2}$	0
000	0	$\frac{1}{2}$	0	$\frac{1}{2}$	0	$\frac{i}{2}$	0	$\frac{-i}{2}$
001	$\frac{1}{2}$	0	$\frac{1}{2}$	0	$\frac{-i}{2}$	0	$\frac{i}{2}$	0
010	$\frac{1}{2}$	0	$\frac{-1}{2}$	0	$\frac{-i}{2}$	0	$\frac{-i}{2}$	0
011	0	$\frac{-1}{2}$	0	$\frac{1}{2}$	0	$\frac{-i}{2}$	0	$\frac{-i}{2}$
100	0	$\frac{-i}{2}$	0	$\frac{-i}{2}$	0	$\frac{-1}{2}$	0	$\frac{1}{2}$
101	$\frac{-i}{2}$	0	$\frac{-i}{2}$	0	$\frac{1}{2}$	0	$\frac{-1}{2}$	0
110	$\frac{-i}{2}$	0	$\frac{i}{2}$	0	$\frac{1}{2}$	0	$\frac{1}{2}$	0
111	0	$\frac{i}{2}$	0	$\frac{-i}{2}$	0	$\frac{1}{2}$	0	$\frac{1}{2}$

- Hadamard gate can be applied directly at qubit  $x_1$

$|x_0\rangle$  \_\_\_\_\_


$|x_1\rangle$  \_\_\_\_\_

$|x_2\rangle$  \_\_\_\_\_

# Running example (Step 1)

$x_2$	000	001	010	011	100	101	110	111
$x_1$	00	01	10	11	00	01	10	11
$x_0$	00	01	10	11	00	01	10	11
000	0	$\frac{1}{\sqrt{2}}$	0	0	0	$\frac{-1}{\sqrt{2}}$	0	0
001	$\frac{1}{\sqrt{2}}$	0	0	0	$\frac{1}{\sqrt{2}}$	0	0	0
010	0	0	$\frac{1}{\sqrt{2}}$	0	0	0	$\frac{1}{\sqrt{2}}$	0
011	0	0	0	$\frac{-1}{\sqrt{2}}$	0	0	0	$\frac{1}{\sqrt{2}}$
100	0	$\frac{-i}{\sqrt{2}}$	0	0	0	$\frac{-i}{\sqrt{2}}$	0	0
101	$\frac{-i}{\sqrt{2}}$	0	0	0	$\frac{i}{\sqrt{2}}$	0	0	0
110	0	0	$\frac{-i}{\sqrt{2}}$	0	0	0	$\frac{i}{\sqrt{2}}$	0
111	0	0	0	$\frac{i}{\sqrt{2}}$	0	0	0	$\frac{i}{\sqrt{2}}$

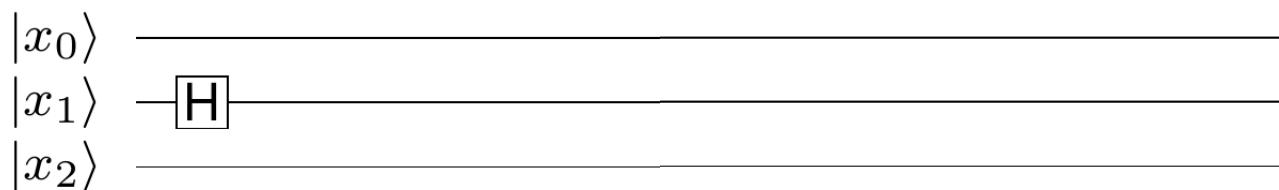- Hadamard gate can **not** be applied directly
- Rearrange columns first
- Align phase shifts
- H gate can be applied at qubit  $x_0$




# Running example (Step 2)

$x_0$	$x_1$	$x_2$	000	001	010	011	100	101	110	111
000	0	0	0	0	0	0	0	1	0	0
001	1	0	0	0	0	0	0	0	0	0
010	0	0	1	0	0	0	0	0	0	0
011	0	0	0	0	0	0	0	0	0	-1
100	0	-i	0	0	0	0	0	0	0	0
101	0	0	0	0	0	-i	0	0	0	0
110	0	0	0	0	0	0	0	0	-i	0
111	0	0	0	i	0	0	0	0	0	0

- No more superposition
- Diagonalize
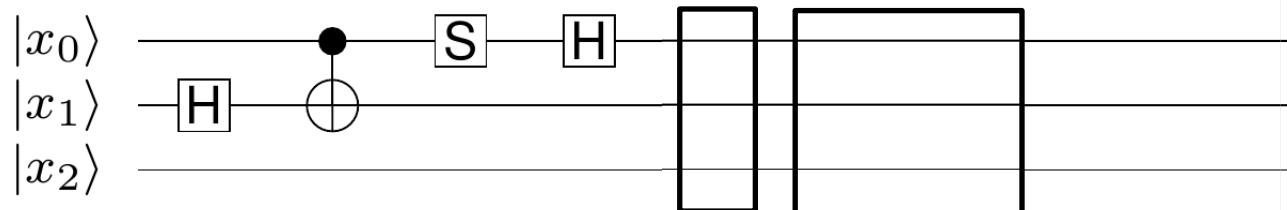
$$\begin{aligned}f_{x_0} &= x_0 \oplus x_2 \\f_{x_1} &= x_1 \\f_{x_2} &= x_1 \oplus x_2\end{aligned}$$




# Running example (Step 3)

$x_2$	000	001	010	011	100	101	110	111
$x_1$	1	0	0	0	0	0	0	0
000	0	1	0	0	0	0	0	0
001	0	0	1	0	0	0	0	0
010	0	0	0	1	0	0	0	0
011	0	0	0	0	1	0	0	0
100	0	0	0	0	0	1	0	0
101	0	0	0	0	0	0	1	0
110	0	0	0	0	0	0	0	1
111	0	0	0	0	0	0	0	0

- Remove phase shifts



Done!

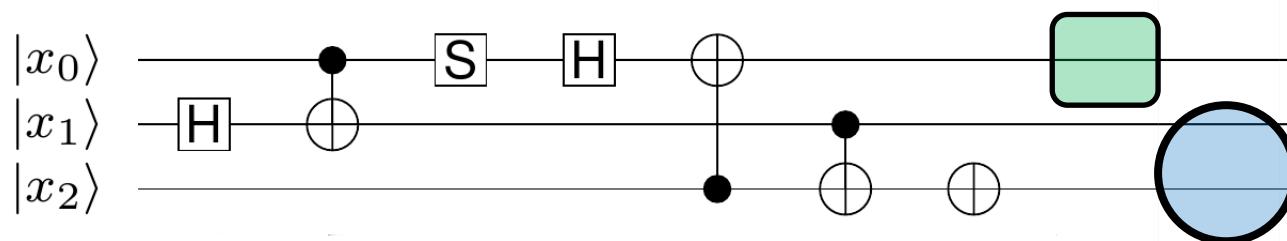

# Complexity and Convergence

- Complexity
  - Matrices grow exponentially!
  - Use of adequate data structures  
(e.g. QMDD, QuIDD)
  
- Convergence
  - Guaranteed by special properties of Clifford Groups
  - Terminates after  $\mathcal{O}(n^2)$  steps

# Experimental Results

[A1] Shende, Bullock, and Markov, "Synthesis of quantum-logic circuits," IEEE Trans. on CAD, vol. 25, no. 6, pp. 1000–1010, 2006.

[A2] Saeedi, Arabzadeh, Zamani, and Sedighi, "Block-based quantum-logic synthesis," *Quantum Information & Computation*, vol. 11, no. 3&4, 2011.

# Conclusion

- Clifford group
  - ✓ Restricted, but powerful
  - ✓ Fault-tolerant gate library
- Synthesis results
  - ✓ Exploits effects of group generators
  - ✓ Significantly better results than generic approaches



# Efficient Synthesis of Quantum Circuits Implementing Clifford Group Operations

**Philipp Niemann, Robert Wille, and Rolf Drechsler**

University of Bremen, Germany

{pniemann,rwille,drechsle}@informatik.uni-bremen.de