#### Toward Optical Probing Resistant Circuits: A Comparison of Logic Styles and Circuit Design Techniques

<u>Sajjad Parvin</u>, Thilo Krachenfels, Shahin Tajik, Jean-Pierre Seifert, Frank Sill Torres, and Rolf Drechsler

Sajjad Parvin, Doctoral Researcher AGRA Group, University of Bremen





#### Agenda

- What is the problem?
- What has been proposed to solve the problem so far?
- How are we trying to address the problem?
- Conclusion



### What is the problem? I


- Meet the market demand
  - $\uparrow SOC complex ↓ yield → FA tools developed$
- An adversary equipped with FA?
- Hijacking information using laser
- On what basis?




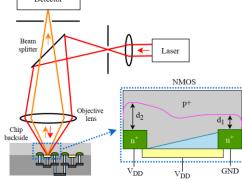
# What is the problem? II

- Silicon  $\rightarrow$  Transparent to NIR
- Go through backside
- As the light passes through the backside
  Modulation of light
- Mainly doping concentration, but




Mobility Minor Bulk Voltage Size Major Voltage Structure
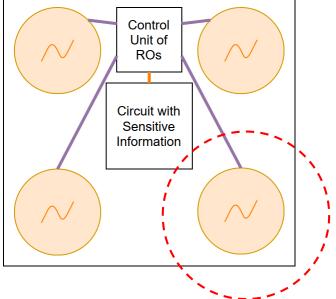
# How to prevent optical probing (Literature) I


- Categorized into 3 types:
  - Sensor-based
  - Change fabrication process of the transistors
  - Circuit level
- Sensor-based\*
  - Active monitoring
  - Large area
  - Can be shut down

Tajik, S., Lohrke, H., Seifert, J. P., & Boit, C. (2017). On the power of optical contactless Probing: Attacking bitstream encryption of FPGAs. Proceedings of the ACM Conference on Computer and Communications Security.


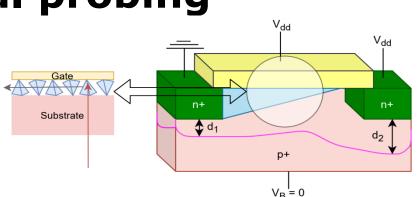
# How to prevent optical probing (Literature) II

- Fabrication based:
  - Opaque layer
    - requires built-in sensors
  - Scramble the light
    - New materials in FET\*
- Circuit level countermeasures
  - Concealing gates
  - Clever circuit designs





### **Circuit level countermeasures I**

- Concealing gates\*
  - Gate obfuscate data
  - Concentration never goes to zero
    - How?
      - Counterpart transistor must switch
- Problem?
  - Multi-input gates
- Solution:
  - Change gate's circuit design
- Concealing Gates NAND2 Gate Target Gate

7

- Propose gates with concealing property

Rahman, M. T., Florida, U., Asadizanjani, N., & Florida, U. (2020). CONCEALING-Gate : Optical Contactless Probing Resilient Design. 1(1), 1–25.



### **Circuit level countermeasures II**

- Let's start on our contribution
  - Formulate the Reflection
  - Proposed several design techniques
  - Experiment on circuits
    - Simulation



#### **Circuit level countermeasures III**


- Magnitude of reflection is:  $RCV = V \times K \times \beta \times P_L \int_0^{2\pi} \int_0^{r_{spot}} p(r) \times A(r, \theta) \, dr d\theta$
- Magnitude of reflection of a FET:

 $RCV_{FET} = RCV_D + RCV_S + RCV_G + e^{-N} \times RCV_{Bulk}$ 

• Magnitude of reflection of a Logic Gate:  $RCV_{Log.Gate} = \sum_{\forall t \in Log.Gate \ i \in \{D, S, G, Bulk\}} RCV_{ti}$ 
 
## **Circuit level countermeasures IV**

- Smaller Area  $\rightarrow$  better
  - Merging diffusion areas
  - 50-75% reduction in area
- Reducing supply power
  - Subthreshold/Near Threshold design
  - Requires on-chip regulator
- Limited output swing
  - No need for voltage regulator
  - Sacrifices the noise margin






#### **Circuit level countermeasures V**

- Inherently obfuscating gates
  - Dual Rail Logic (DRL)
  - How?
- DRL  $\rightarrow$  Both signals
- How well it obfuscate?

#### - CARD

Technology	$C_{min}$	$C_{min}$	$C_{max}$	$C_{max}$
Node (nm)	[*]	ours	[*]	ours
90	0.780	0.208	1.561	0.312
45	0.390	0.104	0.780	0.156
32	0.277	0.074	0.555	0.111
22	0.191	0.051	0.382	0.076

 \*Rahman, M. T., Florida, U., Asadizanjani, N., & Florida, U. (2020). CONCEALING-Gate : Optical Contactless Probing Resilient Design. 1(1), 1–25. 222





A:0, B:0 A:1, B:0 A:0, B:1 A:1, B:1




#### **Circuit level countermeasures IV : Results**

RCV Difference Between Maximum and Minimum Reflection 120 100 PDN PUN 80 PUN + PDN Reflection Difference 60 40 20 0 NAND2 Z N N N N N Z N N ≧ A CMOS CMOS CMOS CMOS CMOS CNTL SRPL DCVS EEPL MCML DCVS NTV STV w/ Lim-DRL PG iter


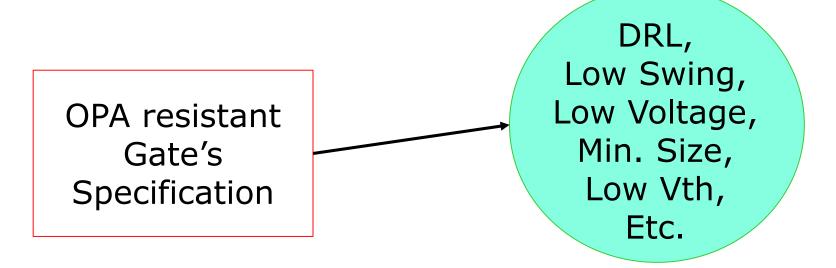
# Conclusion

- Physics of optical probing
- Logic gates and circuit techniques
- Combination of all techniques





# Thank you for you attention! ③

• Questions?